


SCORE JEE (Advanced)

HOME ASSIGNMENT # 02

CAPACITOR

EXERCISE # O-1


1. Ans. (B)

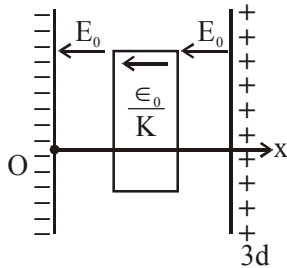

(1) Direction remain same

(2) Potential continuously increase

2. Ans. (D)

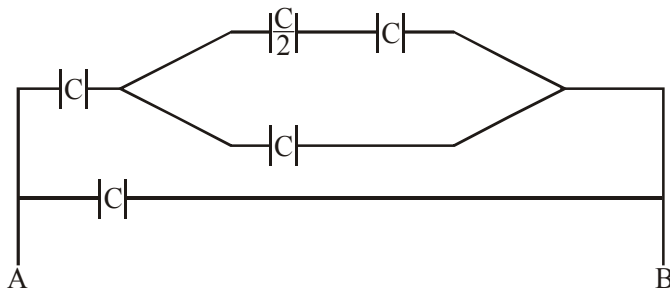


$$C_{eq} = \frac{11C}{7}$$

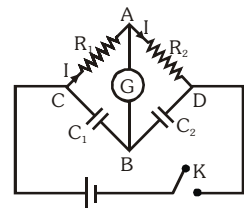3. Ans. (B)

$$\text{as } V_A - V_B = 0, V_C - V_A = IR_1, V_A - V_D = IR_2, V_C - V_B = \frac{Q}{C_1}, V_B - V_A = \frac{Q}{C_2}$$

$$\therefore IR_1 = \frac{Q}{C_1} \dots(i) \quad IR_2 = \frac{Q}{C_2} \dots(ii) \quad \Rightarrow \frac{R_1}{R_2} = \frac{C_2}{C_1}$$



4. **Ans. (B)**

During time ' t_2 ' capacitor is discharging with the help of resistor 'R'

$$\therefore q = q_0 e^{-t/RC}$$

$$V = V_0 e^{-t/RC} \quad [\because Q=CV]$$

$$\text{As } V_0 = \frac{2V}{3}; V = \frac{V}{3}$$

$$t_2 = RC \ln 2$$

During time ' t_1 ' capacitor is charging with the help of battery.

$$\therefore q = q_0 (1 - e^{-t/RC}) \text{ or } V = V_0 (1 - e^{-t/RC})$$

$$\text{as } V_0 = \frac{2V}{3}; V = \frac{V}{3}$$

$$t_1 = RC \ln 2$$

$$T = t_1 + t_2 = 2RC \ln 2$$

5. **Ans. (A)**

$$i = \frac{V}{R} = \frac{V}{\left(\frac{\rho \times d}{S}\right)} = \frac{VS}{\rho d}$$

6. **Ans. (C)**

$$q = 2 \times 5 = 10 \mu\text{C}$$

$$C_{\text{eq}} = 1$$



$$C_{\text{eq}} = \frac{10}{7}$$

$V_{\text{of } 5}$ may be more than 2.

EXERCISE # O-2

1. **Ans. (B, C, D)**

(B) First C increases

(C) $\frac{1}{2} CV^2$ & $\frac{1}{2} \frac{Q^2}{KC}$

(D) $E = \frac{V}{d}$ in both case potential difference across plate is same.

2. **Ans. (A, B, C, D)**

Q – Remain same

Capacitance become KC

3. **Ans. (A, B, C)**

Potential across A & B should same.

$$\frac{V_0}{2} = V_0(1 - e^{-\frac{t}{RC}})$$

4. **Ans. (ABD)**

At $t = 0$, capacitor act a short circuit & current in resistor branch = 0.

At $t = \infty$, $i_R = 2 \text{ mA}$; $i_C = 0$.

Paragraph for question nos. 5 to 7

5. **Ans. (A)**

Electric field will be from A to B

6. **Ans. (D)**


Electric field can be either from A to B or from B to A depending on which is plate is positively charged.

7. **Ans. (C)**

$\int E \cdot d\ell$ is negative of potential difference and it depend on initial and final point.

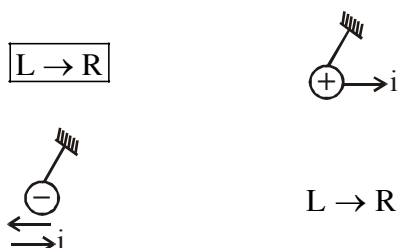8. **Ans. (A)**

Current flow is defined with the flow of charge.



9. Ans. (C)

$$t = \frac{r}{\epsilon_0}$$

$$f = qE$$

$$\text{Work energy} \Rightarrow \frac{1}{2} mV^2 = F \cdot \frac{d}{2}$$



$$\uparrow \frac{V^2}{R}$$

$$T = mg + \frac{mV^2}{R} = mg + \frac{Fd}{R}$$

10. Ans. (B)

$$U_q + U_R = U_0 = \frac{1}{2} \frac{Q^2}{C}$$

$$U_C = U_R$$

$$U_L = \frac{U_0}{2} = \frac{1}{2} \frac{Q^2}{C}$$

11. Ans. (A) P, R, S; (B) P, R, S; (C) R; (D) Q, R]

$$(A) C \rightarrow \frac{C_0}{2}, \quad q = \frac{C_0 V_0}{2}$$

$$C = \frac{AC_0}{2d - d + d/K} = \frac{KC_0}{(K+1)}, \quad V = \frac{Q}{C} = \frac{V_0}{2K}(K+1)$$

(B) Same as A

$$(C) C' = KC_0$$

$$Q = KC_0 V_0$$

$$C_{\text{new}} = \frac{KC_0}{(K+1)}$$

$$V = \frac{KC_0 V_0}{KC_0}(K+1) = V_0(K+1)$$

(D) C' = KC₀

$$C_{\text{new}} = \frac{KC_0}{(K+1)}$$

$$Q = C_{\text{new}} \times V_0 = \frac{KC_0 V_0}{(K+1)}$$

EXERCISE # S


1. **Ans. 9**

Charge on $3\mu\text{F} = 3\mu\text{C}$

Charge on $6\mu\text{F} = 6\mu\text{C}$


by charge conservation = $9\mu\text{C}$

2. **Ans. 8**

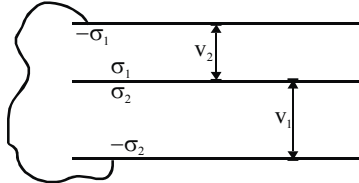

$$V_1 = V_2 \Rightarrow \frac{\sigma_1}{\epsilon_0} \times 5 \times 10^{-2} = \frac{\sigma_2}{\epsilon_0} \times 8 \times 10^{-2} \Rightarrow \frac{\sigma_1}{\sigma_2} = \frac{8}{5}$$

3. **Ans. 30 V**

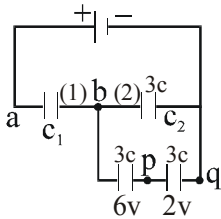

Charge conservation on plates 1, 2 & 3

$$CV = 3C \times 8 + C \times 6$$

$$V = 30$$

4. **Ans. $2 \mu\text{A}$**

$$\frac{Q}{A\epsilon_0} (d - 2 \times 10^{-3} \text{ t}) = \frac{200 - Q}{A\epsilon_0} (d + 2 \times 10^{-3} \text{ t})$$


diff.

$$i(d - 2Vt) + Q(-2V) = -i(d + 2V + t) + (200 - Q)(2V)$$

$$\Rightarrow 2id = 200 \times 2V \times 10^{-6}$$

$$i = 2000 \mu\text{A}$$

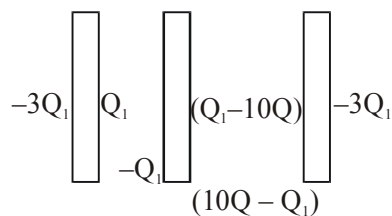
5. **Ans. $-3Q, \frac{+20Q}{3} - \frac{20Q}{3}, \frac{-10Q}{3} + \frac{10Q}{3} - 3Q$**



$$V_A - V_C = 0 = \left(\frac{2Q_1}{2A\epsilon_0} \right) L + \frac{2(Q_1 - 10Q)}{2A\epsilon_0} = 2L$$

$$Q_1 = \frac{20Q}{3}$$

6. **Ans.**

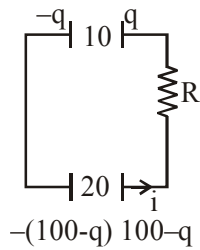

$$-iR - \frac{q}{10} + \frac{100-q}{20} = 0$$

$$iR = 5 + \frac{3q}{20}$$

$$R \frac{dq}{dt} = \frac{3}{20} \left(\frac{100}{3} + q \right)$$

$$q = 200 \left(1 - e^{-\frac{3t}{20R}} \right)$$

7. **Ans.** $V_1 = \frac{C_0 V_0}{C_0 + C_1}$ = common potential

$$V_2 = \frac{C_0 V_1}{(C_0 + C_1)} = \frac{C_0^2 V_1}{(C_0 + C_1)^2}$$

$$V_n = \frac{C_0^n}{(C_0 + C_1)^n} V_0 = V$$

$$\Rightarrow \frac{C_0 + C_1}{C_0} = \left(\frac{V_0}{V} \right)^{1/n}$$

CURRENT ELECTRICITY

EXERCISE # O-1

1. **Ans. (D)**

$C \rightarrow$ Average velocity remain same.


Increase in temperature causes increase in velocity of electrons thus increasing the collision frequency.

2. **Ans. (A)**


Any such black box can be replaced by an effective emf and an effective resistor connected in series. (see fig.)

$\therefore E = I(R + r)$ where E is the effective emf and r is the effective resistance.

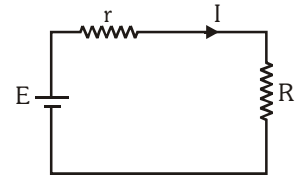Using the given data we find $E = 12$ volts and $r = 2$ ohms. Therefore R should equal 118 ohms in order to get a current of 0.1 amp.



3. **Ans. (A)**

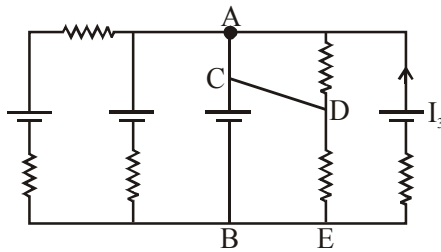

$$V_A - V_B = 2$$

$$I_3 R_3 = 1$$

$$BCDE, \text{ KVL} \Rightarrow R_2 I_2 = 2$$


4. **Ans. (D)**

$$P_1 = P_2 = P_3 = \left(\frac{I}{3}\right)^2 R$$

$$P_4 = \left(\frac{2I}{3}\right)^2 R$$

$$P_5 = \left(\frac{I}{3}\right)^2 R$$

5. **Ans. (B)**

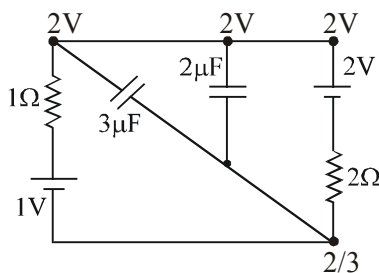

$$V_{\text{across } 3 \mu\text{F}} = 2 - \frac{2}{3} = \frac{4}{3}$$

$$\text{Charge} \Rightarrow q = CV = 4\mu\text{C}$$

6. **Ans. (D)**

We have to take two readings one with resistance R and other without R.
A & B → connection of E is wrong In C → Key should be with R.

7. **Ans. (A)**

$$R_x = \frac{(R_0)(x)}{1-x}; \ln R_x = \ln R_0 + \ln x - \ln (1-x); \frac{dR_x}{R_x} = 0 + \frac{dx}{x} + \frac{dx}{1-x}$$

Systematic error is reduced as effect of cosmelting wire is..... $\frac{dR_x}{R_x}$ is minimum has $x = \frac{1}{2}$

So random error is minimum

EXERCISE # O-2

1. **Ans. (A,B)**



$$R = \int_0^{\ell} \rho x \frac{dx}{\pi \left(r + \frac{rx}{\ell} \right)^2} = \frac{\rho}{\pi r^2}$$

$$\text{Now } R_1 = \int_0^{\ell_1} \rho x \frac{dx}{\pi \left(r + \frac{rx}{\ell} \right)^2} = \frac{\rho}{\pi r^2} \left[\frac{1}{\left(1 + \frac{\ell_1}{\ell} \right)} - 1 \right]$$

$$\frac{1}{1 + \frac{\ell_1}{\ell}} = \frac{3}{4}$$

2. **Ans. (B,D)**

Direction of current from right of left

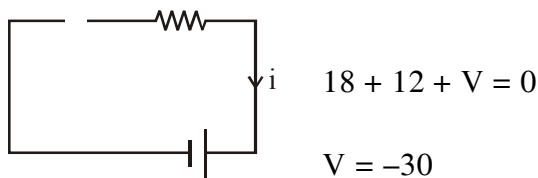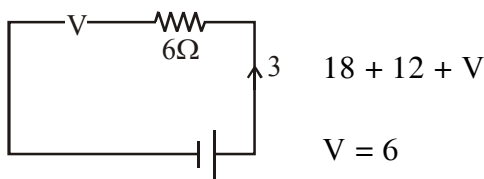

3. **Ans. (B,C,D)**

$i \rightarrow$ will same

$$i = neA V_d$$


$$J = \frac{i}{A}, j^2 \sigma E$$

Current through the wire is same $i_A = i_B = i_C \because i = neAV_d$ and $J = \frac{i}{A}$

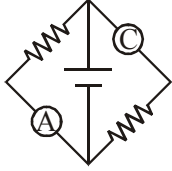4. **Ans. (A)**

Sol. Reading of $C = V$ {i in that branch = 0}


$$\text{Reading of } A = \frac{V}{R} \Rightarrow R$$



$$\frac{V}{V/R} = R$$

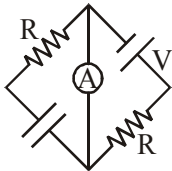
5. **Ans. (D)**

Sol. $V_B = iR_{\text{ammeter}} = 0 \Rightarrow V_{\text{cap.}} = 0$




All current will pass through ammeter


6. **Ans. (C)**

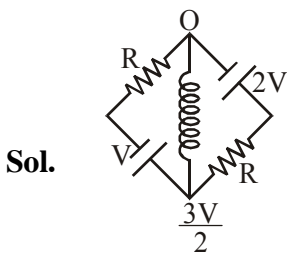

$$i = \frac{V}{2R}$$

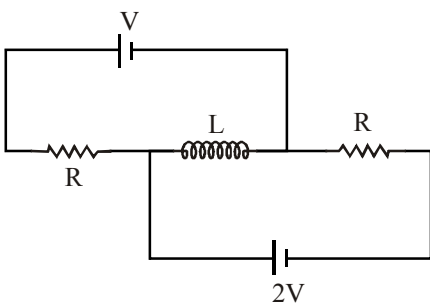


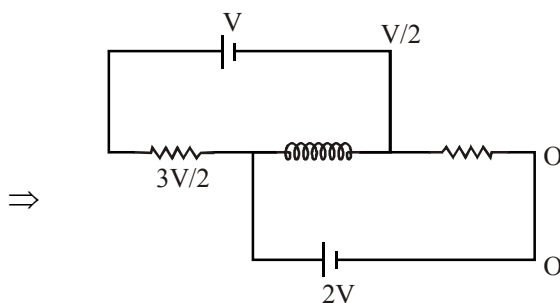at $t = 0$ inductor is open circuit $i = \frac{V}{2R}$



$$\text{p.d. } V - \frac{V}{2} = \frac{3V}{2}$$

7. **Ans. (B)**

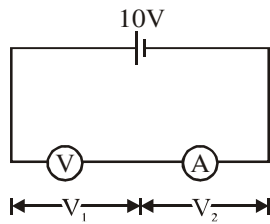


Initially $V_1 + V_2 = 10V \dots(i)$

Finally $\frac{V_1}{3} + 2V_2 = 10V \dots(ii)$

From equation (i) & (ii)

We get $V_1 = 6$ volt, $V_2 = 4$ volt

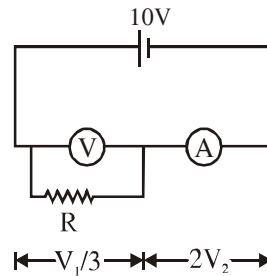\therefore Final reading = $\frac{V_1}{3} = 2$ volt



8. **Ans. (C)**

$$\frac{V_1}{V_2} = \frac{R_A}{R_V} = \frac{4}{6} \text{ \& } R_A = 2\Omega \Rightarrow R_V = 3\Omega$$

9. **Ans. (A)**

$$\frac{\frac{R_V R}{R_V + R}}{R_A} = \frac{\frac{V_1}{3}}{2V_2} = \frac{1}{4} \Rightarrow R = \frac{3}{5}\Omega$$

10. **Ans. (A)**

11. **Ans. (B)**

12. **Ans. (C)**

$$\frac{dR}{R} = \frac{d\ell_1}{\ell_1} + \frac{d\ell_2}{\ell_2}$$

13. **Ans. (B)**

Sol. $\frac{dQ}{dt} = k(T - T_0)$

$$100 = k(40 - 20)$$

$$k = 5 \text{ W/}^\circ\text{C}$$

$$400 = 5(T - 20)$$

$$T = 100^\circ\text{C}$$

So water comes to Boiling point but entire energy is radiated. So it won't boil.

14. **Ans. (B)**

Sol. $\frac{dQ}{dt} = k(T - T_0) = 100 k (40 - 20)$

$$k = 5 \text{ W/}^\circ\text{C}$$

$$\frac{dQ_2}{dt} = k(45 - 20) = 25 \times 5 = 125 \text{ W}$$

15. **Ans. (D)**

Sol. For 1st 60 sec, we can use approx method

$$\frac{dT}{dt} = \frac{k}{ms + C_0} (T_{av} - T_0)$$

$$\frac{5}{60} = \frac{5}{ms + 100} [75.5 - 20]$$

$$\Rightarrow ms + 100 = 3450$$

$$m \times 4200 = 3350$$

16. **Ans. (A) →(P); (B) →(P,R,S,T); (C) →(Q,R,S,T); (D) →(R,T)**

EXERCISE # S

1. **Ans. 5**

All the elements of circuit are in parallel arrangement

$$\frac{1}{R_{eq}} = \frac{1}{40} + \frac{1}{40} + \frac{1}{40} + \frac{1}{40} + \frac{1}{20} + \frac{1}{20} = \frac{4}{40} + \frac{2}{20}; R_{eq} = 5\Omega; \text{Power} = V^2/R = 5 \text{ W}$$


$$m = \frac{3360}{4200} = 0.8 \text{ kg}$$

$$\text{vol.} = \frac{m}{\rho} = \frac{0.8}{1000} \text{ m}^3 = 0.8 \text{ l}$$

2. **Ans. 2**

If $I_G = 0$ then it becomes a balanced whetstone bridge $\ell_1 = \frac{2}{3} \times 1m = \frac{2}{3} \times 100 = \frac{200}{3} \text{ cm}$

3. **Ans. 6**

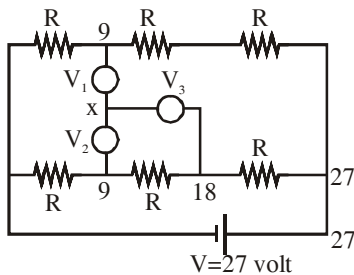

$$\frac{x-9}{R} + \frac{x-9}{R} + \frac{x-18}{R} = 0 \Rightarrow x = 12 \therefore V_3 = 6 \text{ volt}$$

4. **Ans. 3**

$$E_1 = \frac{E \times 40}{100} \text{ and } E_2 = \frac{E \times 40}{100} \Rightarrow \frac{E_1}{E_2} = 1 \Rightarrow \frac{3E_1}{E_2} = 3$$

5. **Ans. 35**

From the given circuit diagram $\frac{R_1}{R_2} = \frac{x^2}{(100)^2 - x^2} \Rightarrow x = 85$

$$\text{Also } \frac{R_2}{R_1} = \frac{y^2}{(100)^2 - y^2} \Rightarrow y = 50$$


$$\Delta = (85 - 50) \text{ cm} = 35 \text{ cm}$$

GEOMETRICAL OPTICS

EXERCISE # O-1

1. **Ans. (A)**
 \therefore Incident angle = reflected angle.

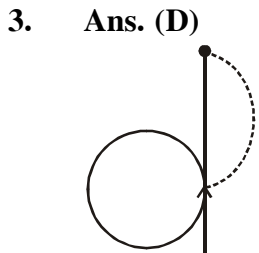2. **Ans. (D)**
 as $u \rightarrow f$ $m \rightarrow \infty$
 as $u \rightarrow \infty$ $m \rightarrow 0$





4. **Ans. (A)**

Optical path = $\int \mu dz = \int_0^A (Az^2 + 1) dz$

Geometrical path = C

$$\text{Extra} = \left(\frac{AC^4}{4} + C \right) - C$$

5. **Ans. (A)**
 Due to refraction.

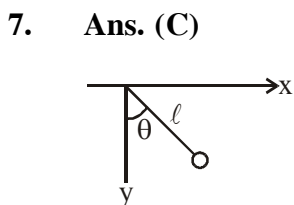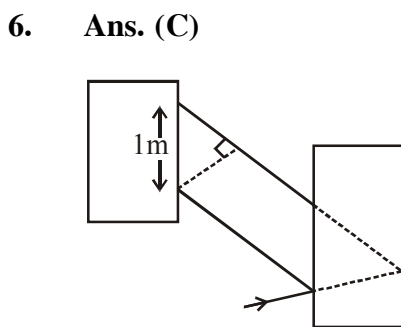


$$\frac{l \cos \theta}{\mu} = y$$

$$l \sin \theta = x$$

$$\cos^2 \theta + \sin^2 \theta = 1$$


8. Ans. (C)

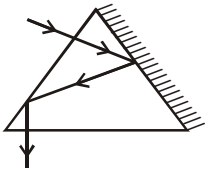

9. Ans. (A)


CORRECTION

Area will be less

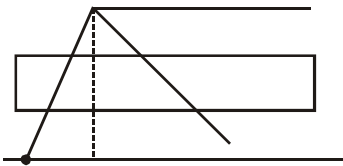

10. Ans. (B)

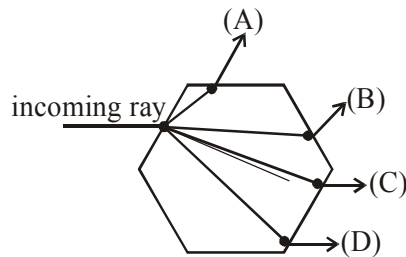11. A light ray strikes a hexagonal ice crystal floating in the air as shown in the figure. The correct path of ray may be ?



Ans. (A)

CORRECTION ANS (C)

12. Ans. (A)

13. Ans. (A)

14. Ans. (C)

15. Ans. (A)

16. Ans. (B)

17. Ans. (A)

18. Ans. (B)

19. Ans. (C)

EXERCISE # O-2

1. Ans. (A,D)

2. Ans. (B,C)

3. Ans. (D)

4. Ans. (C)

5. Ans. (BD)

6. Ans. (ABC)
 7. Ans. (C)
 8. Ans. (B)
 9. Ans. (D)
 10. Ans. (A)

$$\mu_1 \sin r_1 = \sin i_1 \Rightarrow r_1 = \sin^{-1} \left(\frac{\sin i_1}{\mu_1} \right)$$

11. Ans. (A)

$$\frac{\mu_1}{\mu_2} \sin i_2 = \sin r_2; \quad \frac{\mu_1 R_1 \sin i_1}{\mu_2 R_2 \mu_1} = \sin r_2; \quad r_2 = \sin^{-1} \left(\frac{R_1}{\mu_2 R_2} \sin i_1 \right)$$

12. Ans. (BD)
 13. Ans. (A,C,D)
 14. Ans. (A) PQR (B) Q (C) S (D) ST
 15. Ans. (A) PRST (B) Q (C) PQST (D) PRST
 16. Ans. (A,B,C)

EXERCISE # S

1. Ans. $\theta < \sin^{-1}(2 \sin 15^\circ)$
 2. Ans. $\left(\frac{16}{25} \text{ mm} \right)$
 3. Ans. $y = -\frac{x}{1200} + 0.1$
 4. Ans : Real, below principal axis, anywhere b/w P & F₁]
 5. Ans. $\delta_1 = \tan^{-1} \left(\frac{h}{f} - \tan \frac{\theta}{2} \right) + \frac{\theta}{2}$
 $\delta_2 = \tan^{-1} \left(\frac{h}{f} + \tan \frac{\theta}{2} \right) - \frac{\theta}{2}$
 & Angle between rays = $\tan^{-1} \left(\frac{h}{f} + \tan \frac{\theta}{2} \right) - \tan^{-1} \left(\frac{h}{f} - \tan \frac{\theta}{2} \right)$
 6. Ans. $d = 6 \text{ cm}$
 7. Ans. (i) 2° , (ii) $\frac{4\pi}{9} \text{ mm}$
 8. Ans. (i) $\lambda_0 = 600 \text{ nm}$, $n = 1.5$ (ii) $i = \sin^{-1}(0.75) = 48.59^\circ$
 9. Ans. $r_1 = \frac{a}{3}$, $r_2 = \frac{a}{11}$, $r_3 = \frac{a}{50}$
 10. Ans. $\frac{4GM}{Rc^2}$
 11. Ans. (i) $f = -10 \text{ cm}$, (ii) (10, 2)