
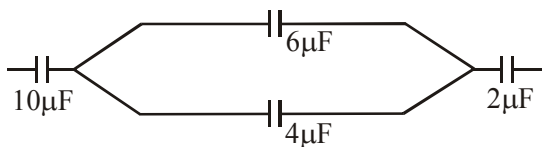


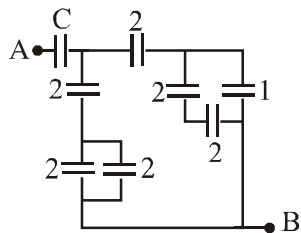


6. In the figure shown below, the charge on the left plate of the  $10\ \mu\text{F}$  capacitor is  $-30\ \mu\text{C}$ . ? The charge on the right plate of the  $6\ \mu\text{F}$  capacitor is :



- (1)  $-18\ \mu\text{C}$                       (2)  $-12\ \mu\text{C}$   
 (3)  $+12\ \mu\text{C}$                       (4)  $+18\ \mu\text{C}$
7. In the circuit shown, find  $C$  if the effective capacitance of the whole circuit is to be  $0.5\ \mu\text{F}$ . All values in the circuit are in  $\mu\text{F}$ .



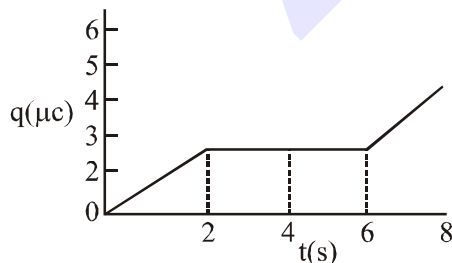- (1)  $\frac{7}{10}\ \mu\text{F}$     (2)  $\frac{7}{11}\ \mu\text{F}$     (3)  $\frac{6}{5}\ \mu\text{F}$     (4)  $4\ \mu\text{F}$
8. The charge on a capacitor plate in a circuit, as a function of time, is shown in the figure: What is the value of current at  $t = 4\ \text{s}$  ?




- (1)  $3\ \mu\text{A}$                               (2)  $2\ \mu\text{A}$   
 (3) zero                                      (4)  $1.5\ \mu\text{A}$

9. A parallel plate capacitor with plates of area  $1\ \text{m}^2$  each, area  $t$  a separation of  $0.1\ \text{m}$ . If the electric field between the plates is  $100\ \text{N/C}$ , the magnitude of charge each plate is :-

(Take  $\epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}$ )

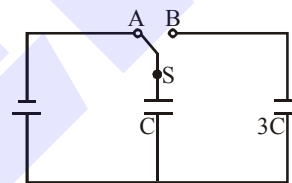- (1)  $7.85 \times 10^{-10}\ \text{C}$   
 (2)  $6.85 \times 10^{-10}\ \text{C}$   
 (3)  $9.85 \times 10^{-10}\ \text{C}$   
 (4)  $8.85 \times 10^{-10}\ \text{C}$
10. In the figure shown, after the switch 'S' is turned from position 'A' to position 'B', the energy dissipated in the circuit in terms of capacitance 'C' and total charge 'Q' is:




- (1)  $\frac{3Q^2}{8C}$                               (2)  $\frac{3Q^2}{4C}$   
 (3)  $\frac{1Q^2}{8C}$                               (4)  $\frac{5Q^2}{8C}$
11. A parallel plate capacitor has  $1\ \mu\text{F}$  capacitance. One of its two plates is given  $+2\ \mu\text{C}$  charge and the other plate,  $+4\ \mu\text{C}$  charge. The potential difference developed across the capacitor is:-
- (1)  $5\ \text{V}$                                       (2)  $2\ \text{V}$   
 (3)  $3\ \text{V}$                                       (4)  $1\ \text{V}$
12. Voltage rating of a parallel plate capacitor is  $500\ \text{V}$ . Its dielectric can withstand a maximum electric field of  $10^6\ \text{V/m}$ . The plate area is  $10^{-4}\ \text{m}^2$ . What is the dielectric constant is the capacitance is  $15\ \text{pF}$ ? (given  $\epsilon_0 = 8.86 \times 10^{-12}\ \text{C}^2/\text{Nm}^2$ )
- (1)  $3.8$                                       (2)  $4.5$   
 (3)  $6.2$                                       (4)  $8.5$

13. The parallel combination of two air filled parallel plate capacitors of capacitance  $C$  and  $nC$  is connected to a battery of voltage,  $V$ . When the capacitors are fully charged, the battery is removed and after that a dielectric material of dielectric constant  $K$  is placed between the two plates of the first capacitor. The new potential difference of the combined system is :-

- (1)  $\frac{V}{K+n}$  (2)  $V$   
 (3)  $\frac{(n+1)V}{(K+n)}$  (4)  $\frac{nV}{K+n}$

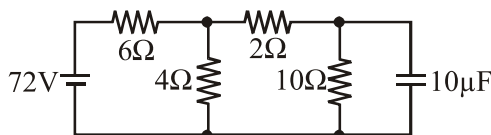14. Determine the charge on the capacitor in the following circuit :




- (1)  $2\mu\text{C}$  (2)  $60\mu\text{C}$   
 (3)  $200\mu\text{C}$  (4)  $10\mu\text{C}$

15. A capacitor with capacitance  $5\mu\text{F}$  is charged to  $5\mu\text{C}$ . If the plates are pulled apart to reduce the capacitance to  $2\mu\text{F}$ , how much work is done ?


- (1)  $3.75 \times 10^{-6} \text{ J}$  (2)  $2.55 \times 10^{-6} \text{ J}$   
 (3)  $2.16 \times 10^{-6} \text{ J}$  (4)  $6.25 \times 10^{-6} \text{ J}$

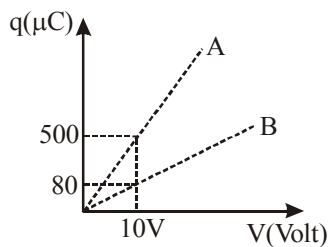16. Figure shows charge ( $q$ ) versus voltage ( $V$ ) graph for series and parallel combination of two given capacitors. The capacitances are :



- (1)  $50 \mu\text{F}$  and  $30 \mu\text{F}$  (2)  $20 \mu\text{F}$  and  $30 \mu\text{F}$   
 (3)  $60 \mu\text{F}$  and  $40 \mu\text{F}$  (4)  $40 \mu\text{F}$  and  $10 \mu\text{F}$

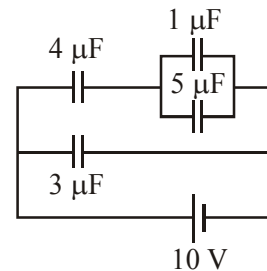
17. In the given circuit, the charge on  $4 \mu\text{F}$  capacitor will be :



- (1)  $5.4 \mu\text{C}$  (2)  $24 \mu\text{C}$   
 (3)  $13.4 \mu\text{C}$  (4)  $9.6 \mu\text{C}$

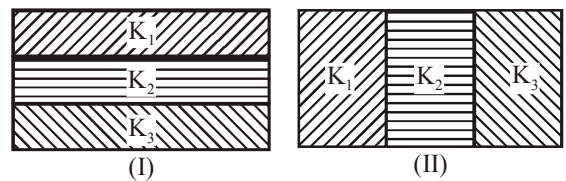18. Two identical parallel plate capacitors, of capacitance  $C$  each, have plates of area  $A$ , separated by a distance  $d$ . The space between the plates of the two capacitors, is filled with three dielectrics, of equal thickness and dielectric constants  $K_1, K_2$  and  $K_3$ . The first capacitor is filled as shown in fig. I, and the second one is filled as shown in fig. II.

If these two modified capacitors are charged by the same potential  $V$ , the ratio of the energy stored in the two, would be ( $E_1$  refers to capacitor (I) and  $E_2$  to capacitor (II)) :




(1)  $\frac{E_1}{E_2} = \frac{9K_1K_2K_3}{(K_1 + K_2 + K_3)(K_2K_3 + K_3K_1 + K_1K_2)}$

(2)  $\frac{E_1}{E_2} = \frac{K_1K_2K_3}{(K_1 + K_2 + K_3)(K_2K_3 + K_3K_1 + K_1K_2)}$

(3)  $\frac{E_1}{E_2} = \frac{(K_1 + K_2 + K_3)(K_2K_3 + K_3K_1 + K_1K_2)}{K_1K_2K_3}$

(4)  $\frac{E_1}{E_2} = \frac{(K_1 + K_2 + K_3)(K_2K_3 + K_3K_1 + K_1K_2)}{9K_1K_2K_3}$

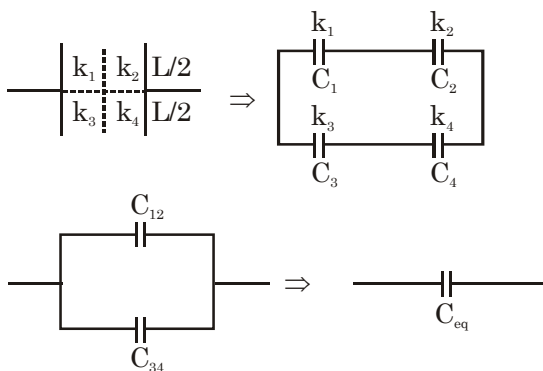**SOLUTION****1. Ans. (Bonus)**

$$C_{12} = \frac{C_1 C_2}{C_1 + C_2} = \frac{k_1 \epsilon_0 \frac{L}{2} \times L \cdot k_2 \left[ \epsilon_0 \frac{L}{2} \times L \right]}{d/2 \cdot \frac{d/2}{(k_1 + k_2) \left[ \frac{\epsilon_0 \cdot \frac{L}{2} \times L}{d/2} \right]}}$$

$$C_{12} = \frac{k_1 k_2 \epsilon_0 L^2}{k_1 + k_2 d}$$

in the same way we get,  $C_{34} = \frac{k_3 k_4 \epsilon_0 L^2}{k_3 + k_4 d}$

$$\therefore C_{eq} = C_{12} + C_{34} = \left[ \frac{k_1 k_2}{k_1 + k_2} + \frac{k_3 k_4}{k_3 + k_4} \right] \frac{\epsilon_0 L^2}{d} \quad \text{..(i)}$$

Now if  $k_{eq} = k$ ,  $C_{eq} = \frac{k \epsilon_0 L^2}{d}$  .....(ii)

on comparing equation (i) to equation (ii), we get

$$k_{eq} = \frac{k_1 k_2 (k_3 + k_4) + k_3 k_4 (k_1 + k_2)}{(k_1 + k_2)(k_3 + k_4)}$$

This does not match with any of the options so probably they have assumed the wrong combination

$$C_{13} = \frac{k_1 \epsilon_0 L \frac{L}{2}}{d/2} + k_3 \epsilon_0 \frac{L \cdot \frac{L}{2}}{d/2}$$

$$= (k_1 + k_3) \frac{\epsilon_0 L^2}{d}$$

$$C_{24} = (k_2 + k_4) \frac{\epsilon_0 L^2}{d}$$


$$C_{eq} = \frac{C_{13} C_{24}}{C_{13} + C_{24}} = \frac{(k_1 + k_3)(k_2 + k_4) \epsilon_0 L^2}{(k_1 + k_2 + k_3 + k_4) d}$$

$$= \frac{k \epsilon_0 L^2}{d}$$

$$k = \frac{(k_1 + k_3)(k_2 + k_4)}{(k_1 + k_2 + k_3 + k_4)}$$

However this is one of the four options.

It must be a "Bonus" logically but of the given options probably they might go with (4)

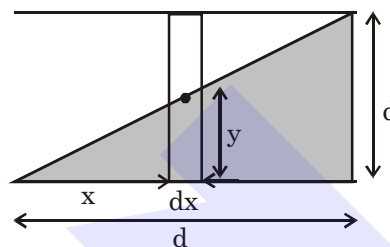**2. Ans. (3)**

$$\frac{y}{x} = \frac{d}{a}$$

$$y = \frac{d}{a} x$$

$$dy = \frac{d}{a} (dx)$$

$$\frac{1}{dc} = \frac{y}{KE \cdot adx} + \frac{(d-y)}{\epsilon_0 adx}$$

$$\frac{1}{dc} = \frac{1}{\epsilon_0 adx} \left( \frac{y}{k} + d - y \right)$$

$$\int dc = \int \frac{\epsilon_0 adx}{\frac{y}{k} + d - y}$$

$$c = \epsilon_0 a \cdot \frac{a}{d} \int_0^d \frac{dy}{d + y \left( \frac{1}{k} - 1 \right)}$$

$$= \frac{\epsilon_0 a^2}{\left( \frac{1}{k} - 1 \right) d} \left[ \ln \left( d + y \left( \frac{1}{k} - 1 \right) \right) \right]_0^d$$

$$= \frac{k \epsilon_0 a^2}{(1-k)d} \ln \left( \frac{d + d \left( \frac{1}{k} - 1 \right)}{d} \right)$$

$$= \frac{k \epsilon_0 a^2}{(1-k)d} \ln \left( \frac{1}{k} \right) = \frac{k \epsilon_0 a^2 \ln k}{(k-1)d}$$

3. **Ans. (3)**

Initial energy of capacitor

$$U_i = \frac{1}{2} \frac{v^2}{c}$$

$$= \frac{1}{2} \times \frac{120 \times 120}{12} = 600 \text{ J}$$

Since battery is disconnected so charge remain same.

Final energy of capacitor

$$U_f = \frac{1}{2} \frac{v^2}{c}$$

$$= \frac{1}{2} \times \frac{120 \times 120}{12 \times 6.5} = 92$$

$$W + U_f = U_i$$

$$W = 508 \text{ J}$$

4. **Ans. (1)**

Let dielectric constant of material used be K.

$$\therefore \frac{10 \epsilon_0 A / 3}{d} + \frac{12 \epsilon_0 A / 3}{d} + \frac{14 \epsilon_0 A / 3}{d} = \frac{K \epsilon_0 A}{d}$$

$$\Rightarrow K = 12$$


5. **Ans. (4)**

$$C_{eq} = \frac{6}{13} \mu\text{F}$$


Therefore three capacitors must be in parallel to get 6 in

$$\frac{1}{C_{eq}} = \frac{1}{3C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C} + \frac{1}{C}$$
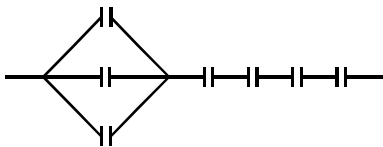
$$C_{eq} = \frac{3C}{13} = \frac{6}{13} \mu\text{F}$$



6. **Ans. (4)**

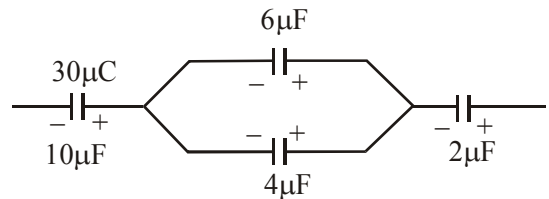

6 $\mu\text{F}$  & 4 $\mu\text{F}$  are in parallel & total charge on this combination is 30  $\mu\text{C}$


$$\therefore \text{Charge on } 6\mu\text{F capacitor} = \frac{6}{6+4} \times 30$$

$$= 18 \mu\text{C}$$

Since charge is asked on right plate therefore is +18 $\mu\text{C}$

Correct answer is (4)

7. **Ans. (2)**

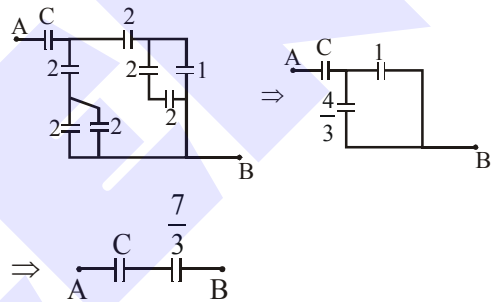

From equs.

$$\frac{7C}{3} = \frac{1}{\frac{7}{3} + C}$$

$$\Rightarrow 14C = 7 + 3C$$

$$\Rightarrow C = \frac{7}{11}$$

8. **Ans. (3)**

9. **Ans. (4)**

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0}$$

$$Q = AE \epsilon_0$$

$$Q = (1)(100)(8.85 \times 10^{-12})$$

$$Q = 8.85 \times 10^{-10} \text{ C}$$


10. **Ans. (1)**

$$V_i = \frac{1}{2} CE^2$$

$$V_f = \frac{(CE)^2}{2 \times 4c} = \frac{1}{2} \frac{CE^2}{4}$$


$$\Delta E = \frac{1}{2} CE^2 \times \frac{3}{4} = \frac{3}{8} CE^2$$

11. Ans. (4)

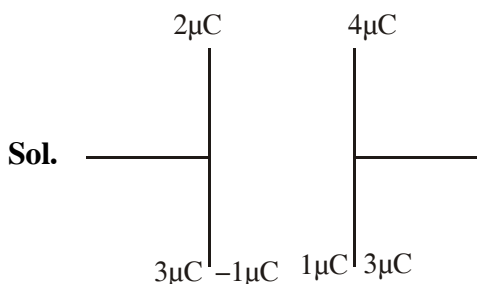Charges at inner plates are  $1\mu\text{C}$  and  $-1\mu\text{C}$  $\therefore$  Potential difference across capacitor

$$= \frac{q}{c} = \frac{1\mu\text{C}}{1\mu\text{F}} = \frac{1 \times 10^{-6}\text{C}}{1 \times 10^{-6}\text{Farad}} = 1\text{V}$$

12. Ans. (4)

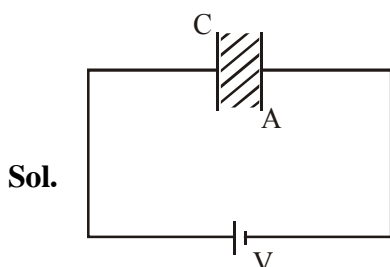

$$A = 10^{-4} \text{ m}^2$$

$$E_{\text{max}} = 10^6 \text{ V/m}$$

$$C = 15 \mu\text{F}$$

$$C = \frac{k\epsilon_0 A}{d}$$


$$\frac{Cd}{\epsilon_0 A} = k$$

$$k = \frac{15 \times 10^{-12} \times 500 \times 10^{-6}}{8.86 \times 10^{-12} \times 10^{-4}}$$

$$= \frac{15 \times 5}{8.86} = 8.465$$

$$k \approx 8.5$$


13. Ans. (3)

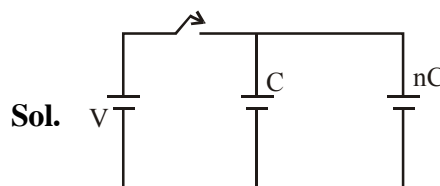

After fully charging, battery is disconnected



$$\begin{aligned} \text{Total charge of the system} &= CV + nCV \\ &= (n+1)CV \end{aligned}$$

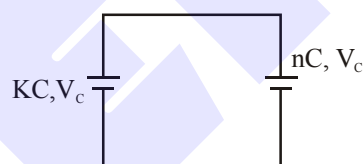After the insertion of dielectric of constant  $K$ 


New potential (common)

$$V_c = \frac{\text{total charge}}{\text{total capacitance}}$$

$$= \frac{(n+1)CV}{KC + nC} = \frac{(n+1)V}{K+n}$$

14. Ans. (3)

Sol. Applying point potential method

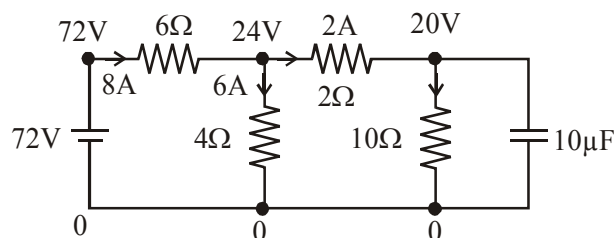

$$q = cV$$

$$q = 10\mu\text{F} \times 20 = 200\mu\text{C}$$

Option (3)

15. Ans. (1)

Sol. Work done =  $\Delta U$

$$\begin{aligned}
 &= U_f - U_i \\
 &= \frac{q^2}{2C_f} - \frac{q^2}{2C_i} \\
 &= \frac{(5 \times 10^{-6})^2}{2} \left( \frac{1}{2 \times 10^{-6}} - \frac{1}{5 \times 10^{-6}} \right) \\
 &= \frac{15}{4} \times 10^{-6} \\
 &= 3.75 \times 10^{-6} \text{ J}
 \end{aligned}$$

Option (1)

16. Ans. (4)

Sol. As  $q = CV$


Hence slope of graph will give capacitance. Slope will be more in parallel combination. Hence capacitance in parallel should be  $50 \mu\text{F}$  & in series combination must be  $8 \mu\text{F}$ .

Only in option  $40 \mu\text{F}$  &  $10 \mu\text{F}$

$$C_{\text{parallel}} = 40 + 10 = 50 \mu\text{F}$$

$$C_{\text{series}} = \frac{40 \times 10}{40 + 10} = 8 \mu\text{F}$$

17. Ans. (2)

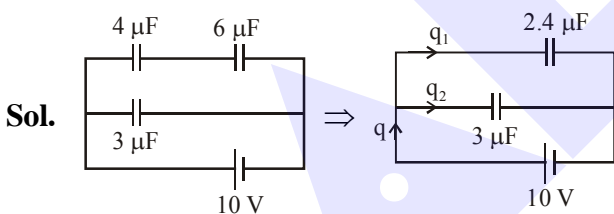

So total charge flow =  $q = 5.4 \mu\text{F} \times 10\text{V}$   
 $= 54 \mu\text{C}$


The charge will be distributed in the ratio of capacitance

$$\Rightarrow \frac{q_1}{q_2} = \frac{2.4}{3} = \frac{4}{5}$$


$$\therefore 9X = 54 \mu\text{C} \Rightarrow X = 6 \mu\text{C}$$

$\therefore$  charge on  $4 \mu\text{F}$  capacitor will be =  $4X = 4 \times 6 \mu\text{C}$   
 $= 24 \mu\text{C}$

18. Ans. (1)

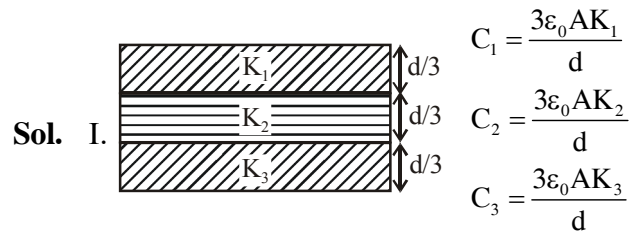
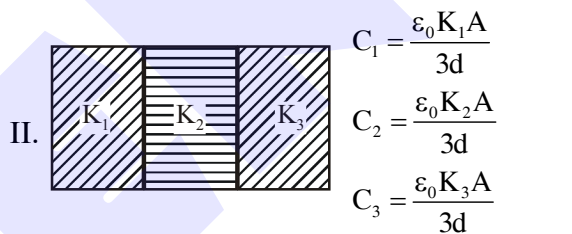
$$\begin{aligned}
 \frac{1}{C_{\text{eq}}} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \\
 \Rightarrow C_{\text{eq}} &= \frac{3\epsilon_0 AK_1 K_2 K_3}{d(K_1 K_2 + K_2 K_3 + K_3 K_1)} \dots\dots(1)
 \end{aligned}$$



$$\begin{aligned}
 C'_{\text{eq}} &= C_1 + C_2 + C_3 \\
 &= \frac{\epsilon_0 A}{3d} (K_1 + K_2 + K_3) \dots\dots(2)
 \end{aligned}$$

Now,

$$\frac{E_1}{E_2} = \frac{\frac{1}{2} C_{\text{eq}} V^2}{\frac{1}{2} C'_{\text{eq}} V^2} = \frac{9K_1 K_2 K_3}{(K_1 + K_2 + K_3)(K_1 K_2 + K_2 K_3 + K_3 K_1)}$$