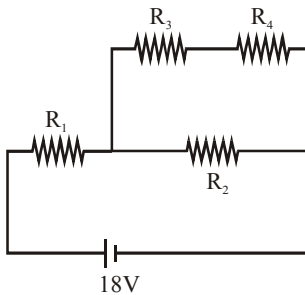


CURRENT ELECTRICITY


1. A carbon resistance has a following colour code. What is the value of the resistance ?




- (1) $1.64 \text{ M}\Omega \pm 5\%$ (2) $530 \text{ k}\Omega \pm 5\%$
 (3) $64 \text{ k}\Omega \pm 10\%$ (4) $5.3 \text{ M}\Omega \pm 5\%$
2. In the given circuit the internal resistance of the 18 V cell is negligible. If $R_1 = 400 \Omega$, $R_3 = 100 \Omega$ and $R_4 = 500 \Omega$ and the reading of an ideal voltmeter across R_4 is 5V, then the value R_2 will be:



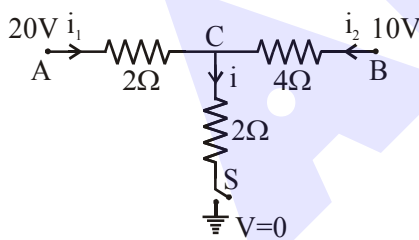- (1) 300Ω (2) 230Ω
 (3) 450Ω (4) 550Ω
3. When the switch S, in the circuit shown, is closed, then the value of current i will be :




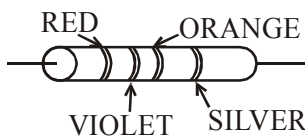- (1) 3 A (2) 5 A (3) 4 A (4) 2 A
4. A resistance is shown in the figure. Its value and tolerance are given respectively by:




- (1) $27 \text{ k}\Omega$, 20% (2) $270 \text{ k}\Omega$, 5%
 (3) $270 \text{ k}\Omega$, 10% (4) $27 \text{ k}\Omega$, 10%

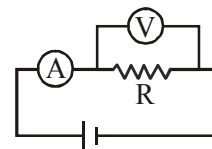5. A copper wire is stretched to make it 0.5% longer. The percentage change in its electrical resistance if its volume remains unchanged is:
 (1) 2.5% (2) 0.5%
 (3) 1.0% (4) 2.0%
6. Drift speed of electrons, when 1.5 A of current flows in a copper wire of cross section 5 mm, is v . If the electron density in copper is $9 \times 10^{28} / \text{m}^3$ the value of v in mm/s is close to (Take charge of electron to be $=1.6 \times 10^{-19} \text{C}$)
 (1) 0.2 (2) 3 (3) 2 (4) 0.02
7. The actual value of resistance R , shown in the figure is 30Ω . This is measured in an experiment as shown using the standard formula $R = \frac{V}{I}$, where V and I are the readings of the voltmeter and ammeter, respectively. If the measured value of R is 5% less, then the internal resistance of the voltmeter is :




- (1) 350Ω (2) 570Ω (3) 35Ω (4) 600Ω
8. A current of 2 mA was passed through an unknown resistor which dissipated a power of 4.4 W. Dissipated power when an ideal power supply of 11V is connected across it is :
 (1) $11 \times 10^{-5} \text{ W}$
 (2) $11 \times 10^{-4} \text{ W}$
 (3) $11 \times 10^5 \text{ W}$
 (4) $11 \times 10^{-3} \text{ W}$

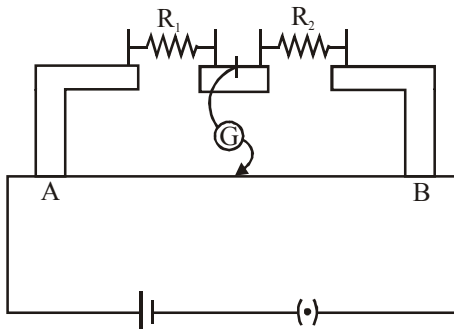15. In the experimental set up of metre bridge shown in the figure, the null point is obtained at a distance of 40 cm from A. If a 10Ω resistor is connected in series with R_1 , the null point shifts by 10 cm. The resistance that should be connected in parallel with $(R_1 + 10)\Omega$ such that the null point shifts back to its initial position is




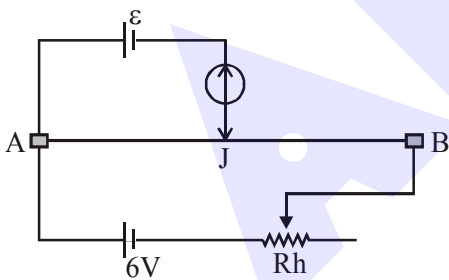- (1) 40Ω (2) 60Ω
 (3) 20Ω (4) 30Ω
16. The resistance of the meter bridge AB is given figure is 4Ω . With a cell of emf $\epsilon = 0.5\text{ V}$ and rheostat resistance $R_h = 2\Omega$ the null point is obtained at some point J. When the cell is replaced by another one of emf $\epsilon = \epsilon_2$ the same null point J is found for $R_h = 6\Omega$. The emf ϵ_2 is;




- (1) 0.6 V (2) 0.5 V
 (3) 0.3 V (4) 0.4 V
17. Two equal resistance when connected in series to a battery, consume electric power of 60 W . If these resistances are now connected in parallel combination to the same battery, the electric power consumed will be :
- (1) 60 W (2) 240 W
 (3) 30 W (4) 120 W

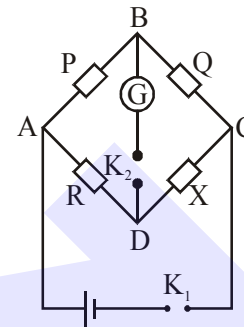18. In a Wheatstone bridge (see fig.), Resistances P and Q are approximately equal. When $R = 400\Omega$, the bridge is equal. When $R = 400\Omega$, the bridge is balanced. On inter-changing P and Q, the value of R, for balance, is 405Ω . The value of X is close to :



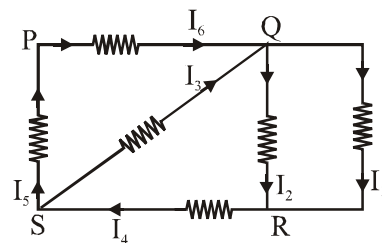- (1) 403.5 ohm (2) 404.5 ohm
 (3) 401.5 ohm (4) 402.5 ohm
19. In the given circuit diagram, the currents, $I_1 = -0.3\text{ A}$, $I_4 = 0.8\text{ A}$ and $I_5 = 0.4\text{ A}$, are flowing as shown. The currents I_2, I_3 and I_6 , respectively, are :



- (1) $1.1\text{ A}, 0.4\text{ A}, 0.4\text{ A}$
 (2) $-0.4\text{ A}, 0.4\text{ A}, 1.1\text{ A}$
 (3) $0.4\text{ A}, 1.1\text{ A}, 0.4\text{ A}$
 (4) $1.1\text{ A}, -0.4\text{ A}, 0.4\text{ A}$
20. A galvanometer, whose resistance is 50 ohm , has 25 divisions in it. When a current of $4 \times 10^{-4}\text{ A}$ passes through it, its needle (pointer) deflects by one division. To use this galvanometer as a voltmeter of range 2.5 V , it should be connected to a resistance of:
- (1) 6250 ohm (2) 250 ohm
 (3) 200 ohm (4) 6200 ohm


21. Two electric bulbs, rated at (25 W, 220 V) and (100 W, 220 V), are connected in series across a 220 V voltage source. If the 25 W and 100 W bulbs draw powers P_1 and P_2 respectively, then:

- (1) $P_1 = 9 \text{ W}$, $P_2 = 16 \text{ W}$
 (2) $P_1 = 4 \text{ W}$, $P_2 = 16 \text{ W}$
 (3) $P_1 = 16 \text{ W}$, $P_2 = 4 \text{ W}$
 (4) $P_1 = 16 \text{ W}$, $P_2 = 9 \text{ W}$

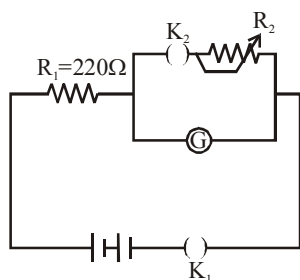22. The galvanometer deflection, when key K_1 is closed but K_2 is open, equals θ_0 (see figure). On closing K_2 also and adjusting R_2 to 5Ω ,

the deflection in galvanometer becomes $\frac{\theta_0}{5}$.

The resistance of the galvanometer is, then, given by [Neglect the internal resistance of battery]:




- (1) 12Ω (2) 25Ω
 (3) 5Ω (4) 22Ω

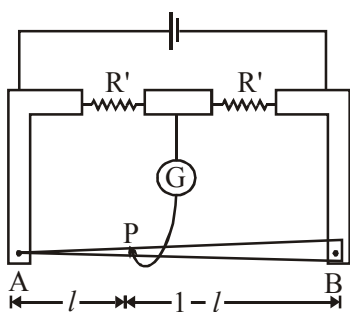23. In a meter bridge, the wire of length 1 m has a non-uniform cross-section such that, the variation $\frac{dR}{dl}$ of its resistance R with length l

is $\frac{dR}{dl} \propto \frac{1}{\sqrt{l}}$. Two equal resistances are

connected as shown in the figure. The galvanometer has zero deflection when the jockey is at point P. What is the length AP?




- (1) 0.25 m (2) 0.3 m
 (3) 0.35 m (4) 0.2 m

24. An ideal battery of 4 V and resistance R are connected in series in the primary circuit of a potentiometer of length 1 m and resistance 5Ω . The value of R , to give a potential difference of 5 mV across 10 cm of potentiometer wire, is :

- (1) 490Ω (2) 480Ω
 (3) 395Ω (4) 495Ω

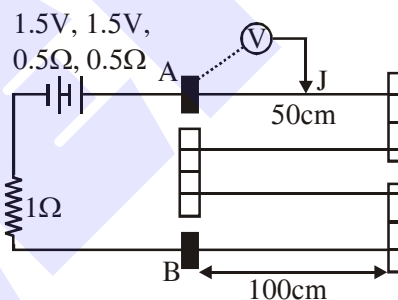25. In the circuit shown, a four-wire potentiometer is made of a 400 cm long wire, which extends between A and B. The resistance per unit length of the potentiometer wire is $r = 0.01\Omega/\text{cm}$. If an ideal voltmeter is connected as shown with jockey J at 50 cm from end A, the expected reading of the voltmeter will be :-




- (1) 0.20 V (2) 0.25 V
 (3) 0.75 V (4) 0.50 V

26. A cell of internal resistance r drives current through an external resistance R . The power delivered by the cell to the external resistance will be maximum when :-

- (1) $R = 1000r$ (2) $R = 0.001r$
 (3) $R = 2r$ (4) $R = r$

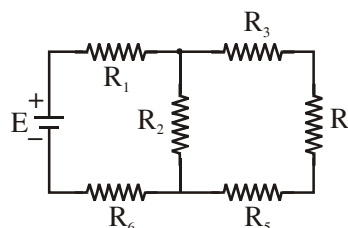
27. In the figure shown, what is the current (in Ampere) drawn from the battery? You are given:

$R_1 = 15\Omega$, $R_2 = 10\Omega$, $R_3 = 20\Omega$, $R_4 = 5\Omega$,
 $R_5 = 25\Omega$, $R_6 = 30\Omega$, $E = 15 \text{ V}$



- (1) $7/18$ (2) $13/24$ (3) $9/32$ (4) $20/3$

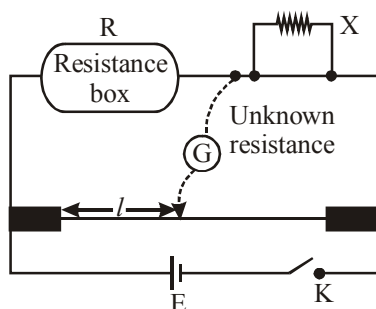
37. In a meter bridge experiment, the circuit diagram and the corresponding observation table are shown in figure



Sl. No.	$R(\Omega)$	$l(\text{cm})$
1.	1000	60
2.	100	13
3.	10	1.5
4.	1	1.0


Which of the readings is inconsistent?

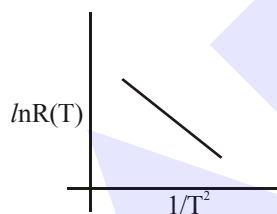- (1) 4 (2) 1 (3) 2 (4) 3
38. In an experiment, the resistance of a material is plotted as a function of temperature (in some range). As shown in the figure, it is a straight line. One may conclude that :



- (1) $R(T) = \frac{R_0}{T^2}$ (2) $R(T) = R_0 e^{-T^2/T_0^2}$
- (3) $R(T) = R_0 e^{-T_0^2/T^2}$ (4) $R(T) = R_0 e^{T^2/T_0^2}$
39. A moving coil galvanometer allows a full scale current of 10^{-4} A. A series resistance of $2 \text{ M}\Omega$ is required to convert the above galvanometer into a voltmeter of range 0-5 V. Therefore the value of shunt resistance required to convert the above galvanometer into an ammeter of range 0-10 mA is :
- (1) 200Ω (2) 100Ω
- (3) 10Ω (4) 500Ω

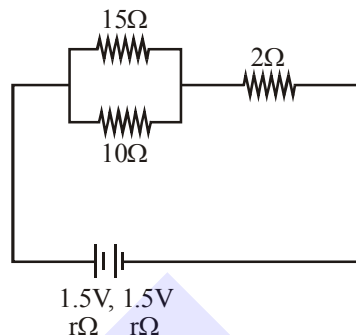40. In the given circuit, an ideal voltmeter connected across the 10Ω resistance reads 2V. The internal resistance r , of each cell is :



- (1) 1Ω (2) 1.5Ω (3) 0Ω (4) 0.5Ω
41. A moving coil galvanometer, having a resistance G , produces full scale deflection when a current I_g flows through it. This galvanometer can be converted into (i) an ammeter of range 0 to I_0 ($I_0 > I_g$) by connecting a shunt resistance R_A to it and (ii) into a voltmeter of range 0 to V ($V = GI_0$) by connecting a series resistance R_V to it. Then,

$$(1) R_A R_V = G^2 \left(\frac{I_g}{I_0 - I_g} \right) \text{ and } \frac{R_A}{R_V} = \left(\frac{I_0 - I_g}{I_g} \right)^2$$


$$(2) R_A R_V = G^2 \text{ and } \frac{R_A}{R_V} = \left(\frac{I_g}{I_0 - I_g} \right)^2$$

$$(3) R_A R_V = G^2 \text{ and } \frac{R_A}{R_V} = \frac{I_g}{(I_0 - I_g)}$$

$$(4) R_A R_V = G^2 \left(\frac{I_0 - I_g}{I_g} \right) \text{ and } \frac{R_A}{R_V} = \left(\frac{I_g}{I_0 - I_g} \right)^2$$




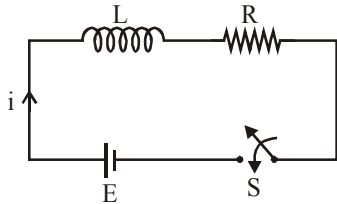
42. Consider the LR circuit shown in the figure. If the switch S is closed at $t = 0$ then the amount of charge that passes through the battery

between $t = 0$ and $t = \frac{L}{R}$ is :





- (1) $\frac{EL}{7.3R^2}$ (2) $\frac{EL}{2.7R^2}$
 (3) $\frac{7.3EL}{R^2}$ (4) $\frac{2.7EL}{R^2}$

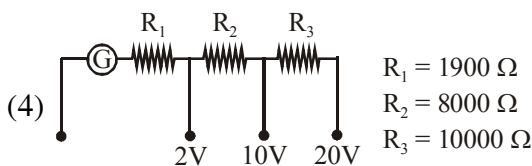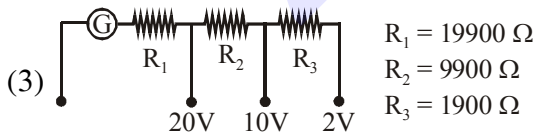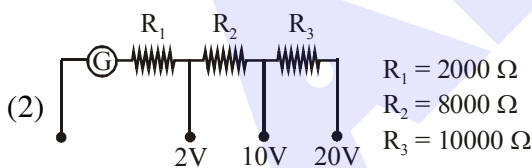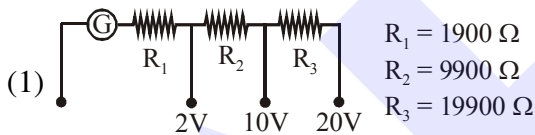43. A galvanometer of resistance 100Ω has 50 divisions on its scale and has sensitivity of $20 \mu\text{A/division}$. It is to be converted to a voltmeter with three ranges, of 0–2 V, 0–10 V and 0–20 V. The appropriate circuit to do so is :




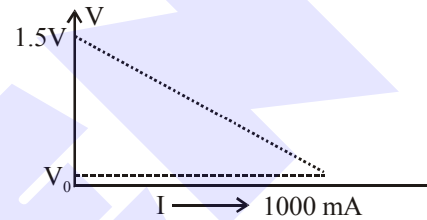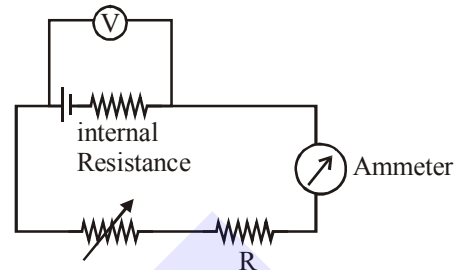44. To verify Ohm's law, a student connects the voltmeter across the battery as, shown in the figure. The measured voltage is plotted as a function of the current, and the following graph is obtained:




If V_0 is almost zero, identify the correct statement:

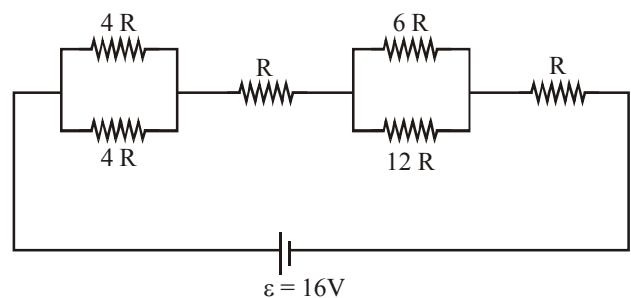
- (1) The value of the resistance R is 1.5Ω
 (2) The emf of the battery is 1.5 V and the value of R is 1.5Ω
 (3) The emf of the battery is 1.5 V and its internal resistance is 1.5Ω
 (4) The potential difference across the battery is 1.5 V when it sends a current of 1000mA .
45. The resistive network shown below is connected to a D.C. source of 16V . The power consumed by the network is 4 Watt . The value of R is :



- (1) 8Ω (2) 6Ω (3) 1Ω (4) 16Ω

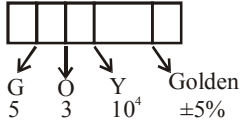SOLUTION1. **Ans. (2)**

$$R = 53 \times 10^4 \pm 5\% = 530 \text{ k}\Omega \pm 5\%$$

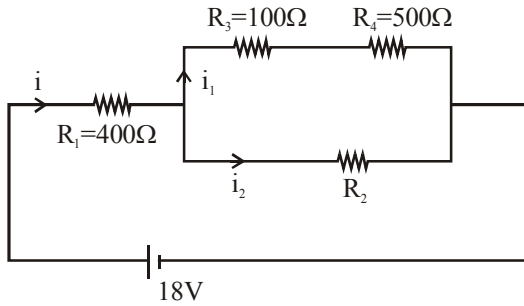2. **Ans. (1)**

$$V_4 = 5V$$

$$i_1 = \frac{V_4}{R_4} = 0.01 \text{ A}$$

$$V_3 = i_1 R_3 = 1V$$

$$V_3 + V_4 = 6V = V_2$$


$$V_1 + V_3 + V_4 = 18V$$

$$V_1 = 12V$$

$$i = \frac{V_1}{R_1} = 0.03 \text{ Amp.}$$

$$i_2 = 0.02 \text{ Amp} \quad V_2 = 6V$$

$$R_2 = \frac{V_2}{i_2} = \frac{6}{0.02} = 300\Omega$$

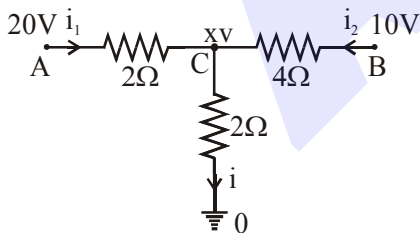3. **Ans. (2)**

Let voltage at C = xv

$$\text{KCL : } i_1 + i_2 = i$$

$$\frac{20-x}{2} + \frac{10-x}{4} = \frac{x-0}{2}$$

$$\Rightarrow x = 10$$

and $i = 5 \text{ amp.}$ 4. **Ans. (4)**

Color code :

Red violet orange silver

$$R = 27 \times 10^3 \Omega \pm 10\%$$

$$= 27 \text{ K}\Omega \pm 10\%$$

5. **Ans. (3)**

$$R = \frac{\rho \ell}{A} \text{ and volume (V)} = A\ell.$$

$$R = \frac{\rho \ell^2}{V}$$

$$\Rightarrow \frac{\Delta R}{R} = \frac{2\Delta \ell}{\ell} = 1\%$$

6. **Ans. (4)**

$$I = neAv_d$$

$$\Rightarrow v_d = \frac{I}{neA} = \frac{1.5}{9 \times 10^{28} \times 1.6 \times 10^{-19} \times 5 \times 10^{-6}}$$

$$= 0.02 \text{ m/s}$$

7. **Ans. (2)**

$$0.95 R = \frac{R R_v}{R + R_v}$$

$$0.95 \times 30 = 0.05 R_v$$

$$R_v = 19 \times 30 = 570 \Omega$$

8. **Ans. (1)**

$$P = I^2 R$$

$$4.4 = 4 \times 10^{-6} R$$

$$R = 1.1 \times 10^6 \Omega$$

$$P' = \frac{11^2}{R} = \frac{11^2}{1.1} \times 10^{-6} = 11 \times 10^{-5} \text{ W}$$

9. **Ans. (2)**

$$R_1 = 32 \times 10 = 320$$

for wheat stone bridge

$$\Rightarrow \frac{R_1}{R_3} = \frac{R_2}{R_4}$$

$$\frac{320}{R_3} = \frac{80}{40}$$


$$R_3 = 160$$

Brown

Blue

Brown

10. Ans. (3)

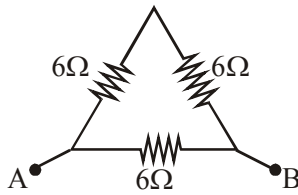

R_{eq} between any two vertex will be

$$\frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{6} \Rightarrow R_{eq} = 4\Omega$$

11. Ans. (4)

$$P = i^2R.$$

\therefore for i_{max} , R must be minimum

from color coding $R = 50 \times 10^2 \Omega$

$$\therefore i_{max} = 20mA$$

12. Ans. (4)

$$i = \frac{\epsilon}{13r}$$

$$i \left(\frac{x}{L} \cdot 12r \right) = \frac{\epsilon}{2}$$

$$\frac{\epsilon}{13r} \left[\frac{x}{L} \cdot 12r \right] = \frac{\epsilon}{2} \Rightarrow \boxed{x = \frac{13L}{24}}$$

13. Ans. (4)

$$i_1 = \frac{10}{20} = 0.5A$$

$$i_2 = 0$$

14. Ans. (4)

Potential difference across AB will be equal to battery equivalent across CD

$$V_{AB} = V_{CD} = \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3}}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}} = \frac{\frac{1}{1} + \frac{2}{1} + \frac{3}{1}}{\frac{1}{1} + \frac{1}{1} + \frac{1}{1}}$$

$$= \frac{6}{3} = 2V$$

15. Ans. (2)

$$\frac{R_1}{R_2} = \frac{2}{3} \dots\dots(i)$$

$$\frac{R_1 + 10}{R_2} = 1 \Rightarrow R_1 + 10 = R_2 \dots\dots(ii)$$

$$\frac{2R_2}{3} + 10 = R_2$$

$$10 = \frac{R_2}{3} \Rightarrow R_2 = 30\Omega$$

$$\& R_1 = 20\Omega$$

$$\frac{30 \times R}{30 + R} = \frac{2}{3}$$

$$R = 60 \Omega$$

16. Ans. (3)

Potential gradient with $R_h = 2\Omega$

$$\text{is } \left(\frac{6}{2+4} \right) \times \frac{4}{L} = \frac{dV}{dL}; L = 100 \text{ cm}$$

Let null point be at ℓ cm

$$\text{thus } \epsilon_1 = 0.5V = \left(\frac{6}{2+4} \right) \times \frac{4}{L} \times \ell \dots(1)$$

Now with $R_h = 6\Omega$ new potential gradient is

$$\left(\frac{6}{4+6} \right) \times \frac{4}{L} \text{ and at null point}$$

$$\left(\frac{6}{4+6} \right) \left(\frac{4}{L} \right) \times \ell = \epsilon_2 \dots(2)$$

dividing equation (1) by (2) we get

$$\frac{0.5}{\epsilon_2} = \frac{10}{6} \text{ thus } \epsilon_2 = 0.3$$

17. Ans. (2)

In series condition, equivalent resistance is $2R$

$$\text{thus power consumed is } 60W = \frac{\epsilon^2}{2R}$$


In parallel condition, equivalent resistance is $R/2$ thus new power is

$$P' = \frac{\epsilon^2}{(R/2)}$$

$$\text{or } P' = 4P = 240W$$

18. Ans. (4)

19. Ans. (1)

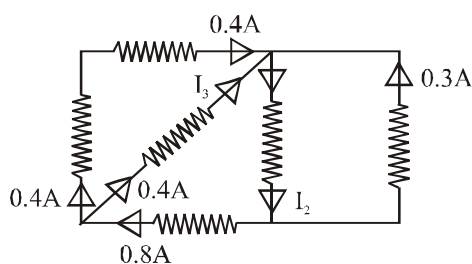
From KCL, $I_3 = 0.8 - 0.4 = 0.4\text{A}$

$$I_2 = 0.4 + 0.4 + 0.3 \\ = 1.1\text{ A}$$

$$I_6 = 0.4\text{A}$$

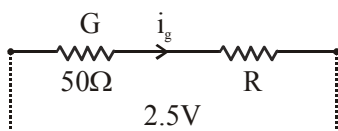20. Ans. (3)

$$I_g = 4 \times 10^{-4} \times 25 = 10^{-2}\text{ A}$$



$$2.5 = (50 + R) 10^{-2} \therefore R = 200\ \Omega$$

21. Ans. (3)

$$R_1 = \frac{220^2}{25}$$

$$R_2 = \frac{220^2}{100}$$

$$L = \frac{220}{R_1 + R_2}$$

$$P_1 = i^2 R_1$$

$$P_2 = i^2 (R_2 = 4\text{W})$$

$$= \frac{220^2}{\left(\frac{220^2}{25} + \frac{220^2}{100}\right)} \times \frac{220^2}{25}$$

$$= \frac{400}{25} = 16\text{W}$$

22. Ans. (4)

$$\text{case I } i_g = \frac{E}{220 + R_g} = C\theta_0 \quad \dots(i)$$

Case II

$$i_g = \left(\frac{E}{220 + \frac{5R_g}{5 + R_g}} \right) \times \frac{5}{(R_g + 5)} = \frac{C\theta_0}{5} \quad \dots(ii)$$

$$\Rightarrow \frac{5E}{225R_g + 1100} = \frac{C\theta_0}{5} \quad \dots(ii)$$

$$\frac{E}{220 + R_g} = C\theta \quad \dots(i)$$

$$\Rightarrow \frac{225R_g + 1100}{1100 + 5R_g} = 5$$

$$\Rightarrow 5500 + 25R_g = 225R_g + 1100$$

$$200R_g = 4400$$

$$R_g = 22\ \Omega$$

Ans. - 4

23. Ans. (1)

For the given wire : $dR = C \frac{dl}{\sqrt{l}}$,where $C = \text{constant}$.Let resistance of part AP is R_1 and PB is R_2

$$\therefore \frac{R_1}{R_2} = \frac{R_1}{R_2} \text{ or } R_1 = R_2 \text{ By balanced}$$

WSB concept.

$$\text{Now } \int dR = c \int \frac{dl}{\sqrt{l}}$$

$$\therefore R_1 = C \int_0^l l^{-1/2} dl = C \cdot 2 \cdot \sqrt{l}$$

$$R_2 = C \int_l^1 l^{-1/2} dl = C \cdot (2 - 2\sqrt{l})$$

Putting $R_1 = R_2$


$$C \cdot 2 \sqrt{l} = C (2 - 2\sqrt{l})$$

$$\therefore 2\sqrt{l} = 1$$

$$\sqrt{l} = \frac{1}{2}$$

$$\text{i.e. } l = \frac{1}{4}\text{ m} \Rightarrow 0.25\text{ m}$$

24. Ans. (3)

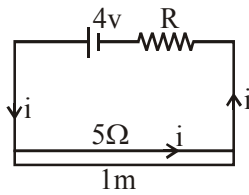

Let current flowing in the wire is i .

$$\therefore i = \left(\frac{4}{R+5} \right) \text{A}$$

If resistance of 10 m length of wire is x

$$\text{then } x = 0.5 \Omega = 5 \times \frac{0.1}{1} \Omega$$


$$\therefore \Delta V = \text{P. d. on wire} = i \cdot x$$

$$5 \times 10^{-3} = \left(\frac{4}{R+5} \right) \cdot (0.5)$$

$$\therefore \frac{4}{R+5} = 10^{-2} \text{ or } R+5 = 400 \Omega$$

$$\therefore R = 395 \Omega$$

25. Ans. (2)

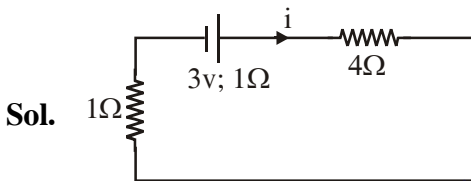

Sol.


Resistance of wire AB = $400 \times 0.01 = 4\Omega$

$$i = \frac{3}{6} = 0.5\text{A}$$

Now voltmeter reading = i (Resistance of 50 cm length)

$$= (0.5\text{A}) (0.01 \times 50) = 0.25 \text{ volt}$$

26. Ans. (4)

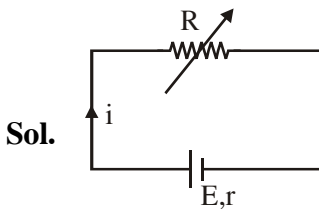

Sol.

$$\text{Current } i = \frac{E}{r+R}$$

Power generated in R

$$P = i^2 R$$


$$P = \frac{E^2 R}{(r+R)^2}$$

for maximum power $\frac{dP}{dR} = 0$



$$E^2 \left[\frac{(r+R)^2 \times 1 - R \times 2(r+R)}{(r+R)^4} \right] = 0$$

$$\Rightarrow r = R$$

27. Ans. (3)

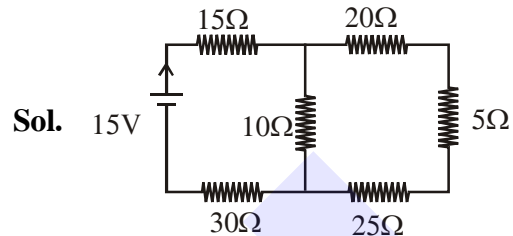

Sol.

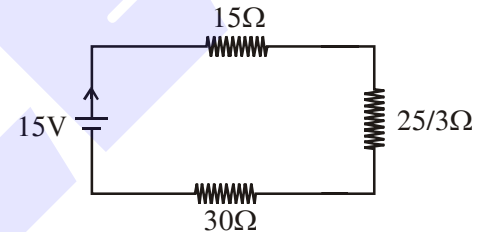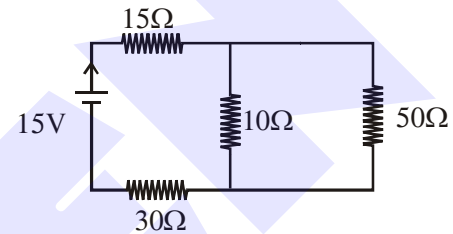

$$R_{eq} = 15 + \frac{25}{3} + 30 = \frac{45 + 25 + 90}{3} = \frac{160}{3}$$

$$I = \frac{E}{R_{eq}} = \frac{15 \times 3}{160} = \frac{9}{32} \text{ amp.}$$

28. Ans. (2)

$$\text{Sol. } E_{eq} = \frac{\frac{E_1}{2R_1} + \frac{E_2}{R_2} + \frac{E_3}{2R_1}}{\frac{1}{2R_1} + \frac{1}{R_2} + \frac{1}{2R_1}}$$


$$= \frac{\frac{2}{2} + \frac{4}{2} + \frac{4}{2}}{\frac{1}{2} + \frac{1}{2} + \frac{1}{2}}$$

$$= \frac{5}{\frac{3}{2}} = \frac{10}{3} = 3.3$$

29. Ans. (3)

Sol. When red is replaced with green 1st digit changes to 5 so new resistance will be 500Ω

30. Ans. (2)

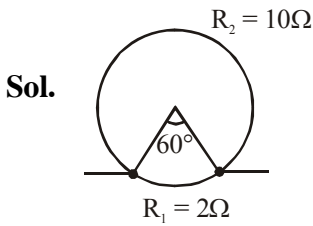

$$R = \frac{\rho \ell^2}{A \ell D} d = \frac{\rho d \ell^2}{m}$$


$$R \propto \ell^2$$

$$R = 12\Omega \text{ (new resistance of wire)}$$

$$R_1 = 2\Omega \quad R_2 = 10\Omega$$

$$R_{eq} = \frac{10 \times 2}{10 + 2} = \frac{5}{3} \Omega.$$

31. Ans. (1)

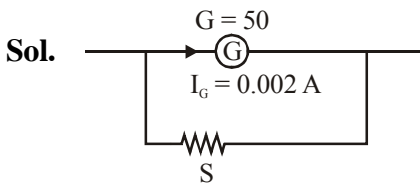

$$S(0.5 - 0.002) = 50 \times 0.002$$

$$S = \frac{50 \times 0.002}{(0.5 - 0.002)} = \frac{0.1}{0.498} = 0.2$$


32. Ans. (4)

Sol.

$$\rho = \frac{m}{ne^2 \tau}$$

$$= 1.67 \times 10^{-8} \Omega \text{m}$$

33. Ans. (3)

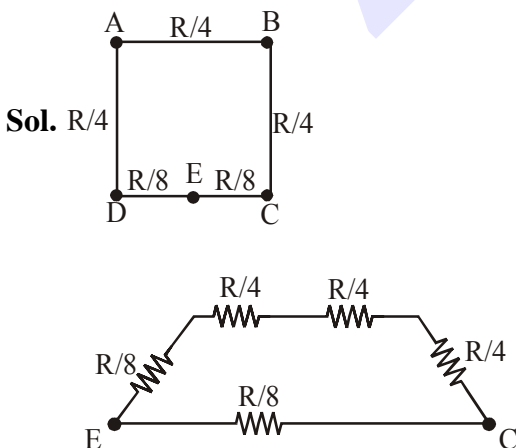

$$\frac{1}{R_{eq}} = \frac{8}{7R} + \frac{8}{R}$$

$$\frac{1}{R_{eq}} = \frac{8 + 56}{7R}$$

$$R_{eq} = \frac{7R}{64}$$

Option (3)

34. Ans. (2)

Sol.

$$G = 50 \Omega$$

$$S = 5000 \Omega$$

$$i_g = 4 \times 10^{-3}$$

$$V = i_g (G + S)$$

$$V = 4 \times 10^{-3} (50 + 5000)$$

$$= 4 \times 10^{-3} (5050)$$

$$= 20.2 \text{ volt}$$

Option (2)

35. Ans. (1)


Sol.

$$dR = \rho \cdot \frac{dx}{4\pi x^2}$$

$$\int dR = \rho \cdot \int_a^b \frac{dx}{4\pi x^2}$$

$$R = \frac{\rho}{4\pi} \left[-\frac{1}{x} \right]_a^b$$
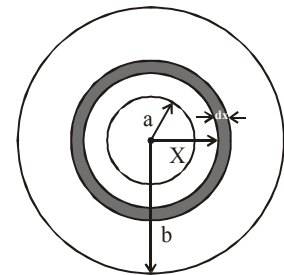
$$R = \frac{\rho}{4\pi} \left(\frac{1}{a} - \frac{1}{b} \right)$$



36. Ans. (4)

Sol.

$$\mu = \frac{V_d}{E} \quad E = \rho J$$

$$= \frac{1.1 \times 10^{-3}}{1.7 \times 10^{-8} \times \frac{5}{\pi \times 25 \times 10^{-6}}}$$

$$= \frac{1.1 \times 10^{-3} \times \pi \times 25 \times 10^{-6}}{1.7 \times 10^{-8} \times 5} \approx 1.01 \text{ m}^2 / \text{Vs}$$

37. Ans. (1)

Sol. as $x = \frac{R(100 - \ell)}{\ell}$

for (1) $x = \frac{1000 \times (100 - 60)}{40} \approx 667$

for (2) $x = \frac{100 \times (100 - 13)}{13} \approx 669$


for (3) $x = \frac{10 \times (100 - 1.5)}{98.5} \approx 656$

for (4) $x = \frac{1 \times (100 - 1)}{1} \approx 95$

So option (4) is completely different hence correct Ans. (4)

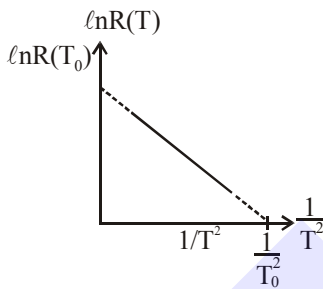38. Ans. (3)

Sol. $\frac{1}{T^2} + \frac{\ell \ln(T)}{\ln R(T)} = 1$
 $\frac{1}{T_0^2} + \frac{\ell \ln(T_0)}{\ln R(T_0)}$



$\Rightarrow \ln R(T) = [\ln R(T_0)] \left(1 - \frac{T_0^2}{T^2} \right)$

$\Rightarrow R(T) = R_0 e^{\left(-\frac{T_0^2}{T^2} \right)}$

39. Ans. (Bonus)

Sol. $200 + 10^{-4} G = 5$

$G = -ve$

So answer is Bonus

40. Ans. (4)

Sol. $R_{eq} = \frac{15 \times 10}{25} + 2 + 2r$

$= 8 + 2r$

$i = \frac{3}{8 + 2r}$


$2 = i R_{eq} = \frac{3}{8 + 2r} \times 6$

$16 + 4r = 18$

$\Rightarrow r = 0.5 \Omega$

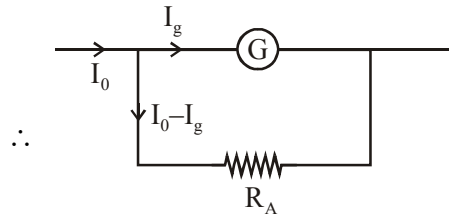41. Ans. (2)

Sol. When galvanometer is used as an ammeter shunt is used in parallel with galvanometer.



$\therefore I_g G = (I_0 - I_g) R_A$

$\therefore R_A = \left(\frac{I_g}{I_0 - I_g} \right) G$

When galvanometer is used as a voltmeter, resistance is used in series with galvanometer.



$I_g (G + R_V) = V = GI_0$ (given $V = GI_0$)

$\therefore R_V = \frac{(I_0 - I_g) G}{I_g}$

$\therefore R_A R_V = G^2$ & $\frac{R_A}{R_V} = \left(\frac{I_g}{I_0 - I_g} \right)^2$

42. Ans. (2)

Sol. $q = \int I dt$

$q = \int_0^{L/R} \frac{E}{R} \left[1 - e^{-\frac{Rt}{L}} \right] dt$

$q = \frac{EL}{R^2} \frac{1}{e}$

$q = \frac{EL}{2.7R^2}$

43. Ans. (4)

Sol. $20 \times 50 \times 10^{-6} = 10^{-3}$ Amp.

$$V_1 = \frac{2}{10^{-3}} = 100 + R_1$$

$$1900 = R_1$$


$$V_2 = \frac{10}{10^{-3}} = (2000 + R_2)$$

$$R_2 = 8000$$

$$V_3 = \frac{20}{10^{-3}} = 10 \times 10^3 + R_3$$

$$10 \times 10^3 = R_3$$

44. Ans. (3)

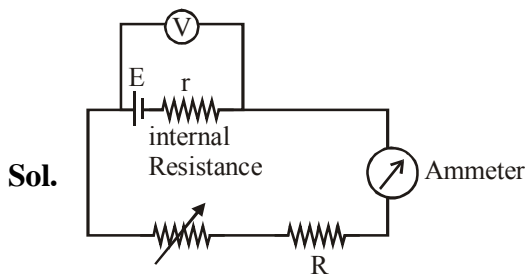

$$V = E - Ir$$


$$\text{when } V = V_0 = 0 \Rightarrow 0 = E - Ir$$

$$\therefore E = r$$

$$\text{when } I = 0, V = E = 1.5\text{V}$$

$$\therefore r = 1.5\Omega.$$

45. Ans. (1)

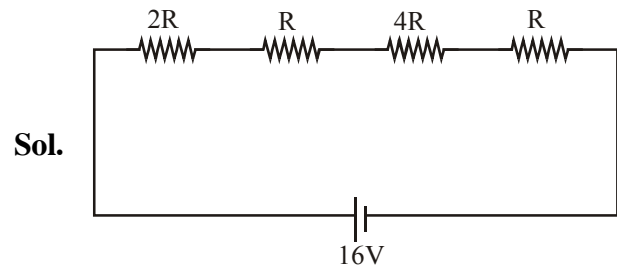

$$P = \frac{16^2}{8R} = 4 \therefore R = 8\Omega$$