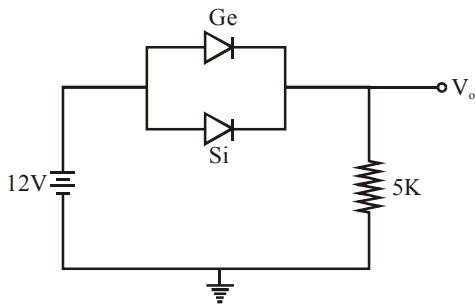


**SEMICONDUCTOR**

1. Ge and Si diodes start conducting at 0.3 V and 0.7 V respectively. In the following figure if Ge diode connection are reversed, the value of  $V_o$  changes by : (assume that the Ge diode has large breakdown voltage)




- (1) 0.6 V                      (2) 0.8 V  
 (3) 0.4 V                      (4) 0.2 V

2. Mobility of electrons in a semiconductor is defined as the ratio of their drift velocity to the applied electric field. If, for an n-type semiconductor, the density of electrons is  $10^{19} \text{m}^{-3}$  and their mobility is  $1.6 \text{m}^2/(\text{V}\cdot\text{s})$  then the resistivity of the semiconductor (since it is an n-type semiconductor contribution of holes is ignored) is close to:


- (1)  $2\Omega\text{m}$   
 (2)  $0.4\Omega\text{m}$   
 (3)  $4\Omega\text{m}$   
 (4)  $0.2\Omega\text{m}$

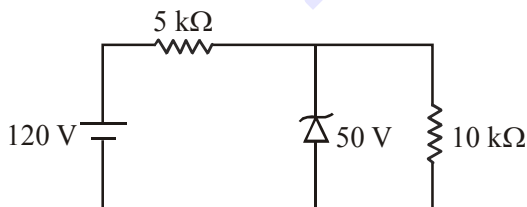3. For the circuit shown below, the current through the Zener diode is :




- (1) 5 mA  
 (2) Zero  
 (3) 14 mA  
 (4) 9 mA

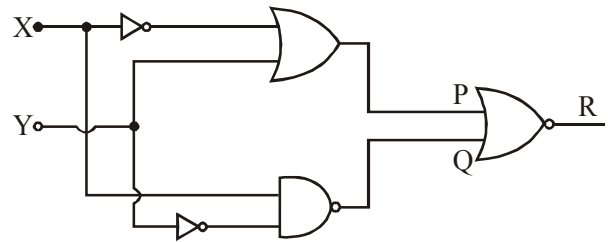4. To get output '1' at R, for the given logic gate circuit the input values must be :




- (1)  $X = 0, Y = 1$   
 (2)  $X = 1, Y = 1$   
 (3)  $X = 0, Y = 0$   
 (4)  $X = 1, Y = 0$

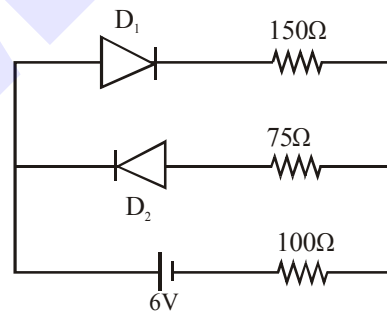5. The circuit shown below contains two ideal diodes, each with a forward resistance of  $50\Omega$ . If the battery voltage is 6 V, the current through the  $100\Omega$  resistance (in Amperes) is :-




- (1) 0.027                      (2) 0.020  
 (3) 0.030                      (4) 0.036

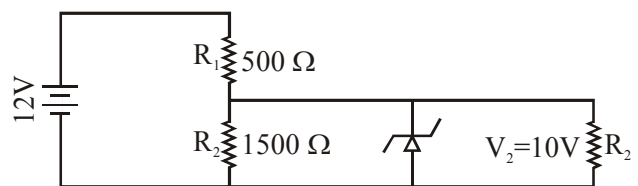6. In the given circuit the current through Zener Diode is close to :



- (1) 6.0 mA                      (2) 4.0 mA  
 (3) 6.7 mA                      (4) 0.0 mA


7.

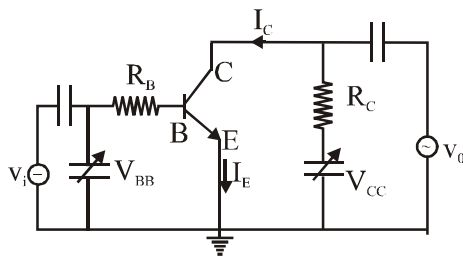

In the figure, given that  $V_{BB}$  supply can vary from 0 to 5.0 V,  $V_{CC} = 5\text{V}$ ,  $\beta_{dc} = 200$ ,  $R_B = 100\text{ k}\Omega$ ,  $R_C = 1\text{ k}\Omega$  and  $V_{BE} = 1.0\text{ V}$ . The minimum base current and the input voltage at which the transistor will go to saturation, will be, respectively :


- (1)  $20\mu\text{A}$  and 3.5V
- (2)  $25\mu\text{A}$  and 3.5V
- (3)  $25\mu\text{A}$  and 2.8V
- (4)  $20\mu\text{A}$  and 2.8V

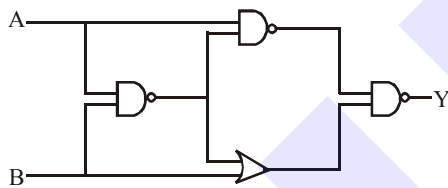8. The output of the given logic circuit is :




- (1)  $\bar{A}B$
- (2)  $A\bar{B}$
- (3)  $AB + \bar{A}\bar{B}$
- (4)  $A\bar{B} + \bar{A}B$

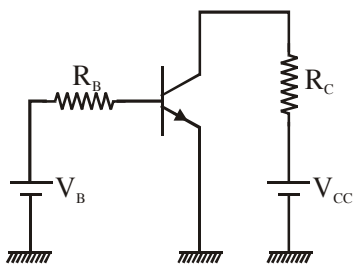9. A common emitter amplifier circuit, built using an npn transistor, is shown in the figure. Its dc current gain is 250,  $R_C = 1\text{ k}\Omega$  and  $V_{CC} = 10\text{ V}$ . What is the minimum base current for  $V_{CE}$  to reach saturation ?



- (1)  $100\mu\text{A}$
- (2)  $7\mu\text{A}$
- (3)  $40\mu\text{A}$
- (4)  $10\mu\text{A}$

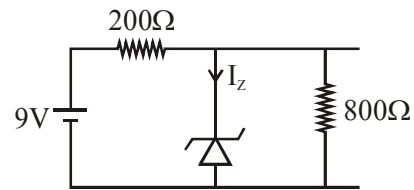
10. The reverse breakdown voltage of a Zener diode is 5.6 V in the given circuit.



The current  $I_Z$  through the Zener is :

- (1) 7 mA
- (2) 17 mA
- (3) 10 mA
- (4) 15 mA

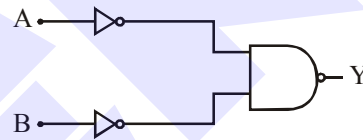11. The logic gate equivalent to the given logic circuit is :-




- (1) OR
- (2) AND
- (3) NOR
- (4) NAND

12. An NPN transistor is used in common emitter configuration as an amplifier with  $1\text{ k}\Omega$  load resistance. Signal voltage of 10 mV is applied across the base-emitter. This produces a 3 mA change in the collector current and  $15\mu\text{A}$  change in the base current of the amplifier. The input resistance and voltage gain are :

- (1)  $0.33\text{ k}\Omega$ , 1.5
- (2)  $0.67\text{ k}\Omega$ , 200
- (3)  $0.33\text{ k}\Omega$ , 300
- (4)  $0.67\text{ k}\Omega$ , 300

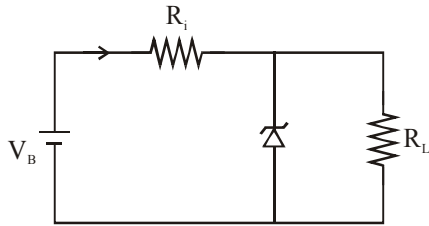
13. The figure represents a voltage regulator circuit using a Zener diode. The breakdown voltage of the Zener diode is 6V and the load resistance is  $R_L = 4\text{ k}\Omega$ . The series resistance of the circuit is  $R_i = 1\text{ k}\Omega$ . If the battery voltage  $V_B$  varies from 8V to 16V, what are the minimum and maximum values of the current through Zener diode ?



- (1) 0.5 mA ; 6 mA    (2) 0.5 mA ; 8.5 mA  
 (3) 1.5 mA ; 8.5 mA    (4) 1 mA ; 8.5 mA
14. An npn transistor operates as a common emitter amplifier, with a power gain of 60 dB. The input circuit resistance is  $100\Omega$  and the output load resistance is  $10\text{ k}\Omega$ . The common emitter current gain  $\beta$  is :


- (1) 60    (2)  $10^4$     (3)  $6 \times 10^2$     (4)  $10^2$

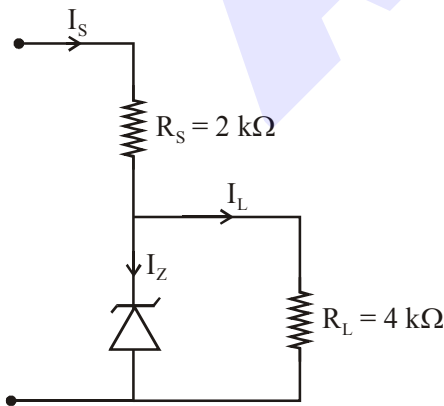15. Figure shown a DC voltage regulator circuit, with a Zener diode of breakdown voltage = 6V. If the unregulated input voltage varies between 10 V to 16 V, then what is the maximum Zener current ?



- (1) 2.5 mA    (2) 3.5 mA  
 (3) 7.5 mA    (4) 1.5 mA

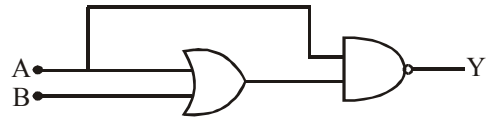16. The truth table for the circuit given in the fig. is:



(1) 

A	B	Y
0	0	1
0	1	1
1	0	0
1	1	0

      (2) 

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	1


(3) 

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

      (4) 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	1

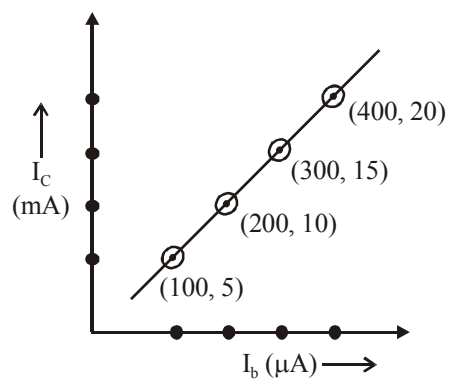17. The transfer characteristic curve of a transistor, having input and output resistance  $100\Omega$  and  $100\text{ k}\Omega$  respectively, is shown in the figure. The Voltage and Power gain, are respectively:



- (1)  $5 \times 10^4$ ,  $5 \times 10^5$   
 (2)  $5 \times 10^4$ ,  $5 \times 10^6$   
 (3)  $5 \times 10^4$ ,  $2.5 \times 10^6$   
 (4)  $2.5 \times 10^4$ ,  $2.5 \times 10^6$

**SOLUTION****1. Ans. (3)**

Initially Ge & Si are both forward biased so current will effectively pass through Ge diode with a drop of 0.3 V

if "Ge" is reversed then current will flow through "Si" diode hence an effective drop of  $(0.7 - 0.3) = 0.4$  V is observed.

**2. Ans. (2)**

$$j = \sigma E = nev_d$$

$$\sigma = ne \frac{v_d}{E}$$

$$= ne\mu$$

$$\frac{1}{\sigma} = \rho = \frac{1}{n_e e \mu_e}$$

$$= \frac{1}{10^{19} \times 1.6 \times 10^{-19} \times 1.6}$$

$$= 0.4 \Omega\text{m}$$


**3. Ans. (4)**

Assuming zener diode doesnot undergo

$$\text{breakdown, current in circuit} = \frac{120}{15000} = 8\text{mA}$$

$$\therefore \text{Voltage drop across diode} = 80\text{V} > 50\text{V.}$$

The diode undergo breakdown.

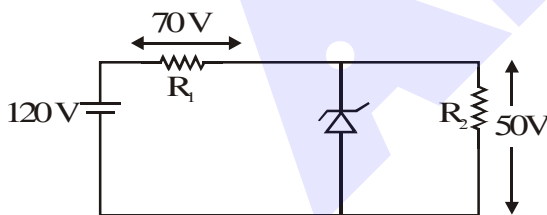

$$\text{Current in } R_1 = \frac{70}{5000} = 14\text{mA}$$

$$\text{Current in } R_2 = \frac{50}{10000} = 5\text{mA}$$

$$\therefore \text{Current through diode} = 9\text{mA}$$

**4. Ans. (4)**

$$p = \bar{x} + y$$

$$Q = \overline{\bar{y}.x} = y + \bar{x}$$

$$O/P = \overline{P+Q}$$

To make O/P

P + Q must be 'O'

$$\text{SO, } y = 0$$

$$x = 1$$

**5. Ans. (2)**

$$I = \frac{6}{300} = 0.002 \text{ (D}_2 \text{ is in reverse bias)}$$

**6. Ans. (4)**

Since voltage across zener diode must be less than 10V therefore it will not work in breakdown region, & its resistance will be infinite & current through it = 0

$\therefore$  correct answer is (4)

**7. Ans (2)**

At saturation,  $V_{CE} = 0$

$$V_{CE} = V_{CC} - I_C R_C$$

$$\Rightarrow I_C = \frac{V_{CC}}{R_C} = 5 \times 10^{-3} \text{ A}$$

Given

$$\beta_{dc} = \frac{I_C}{I_B}$$

$$I_B = \frac{5 \times 10^{-3}}{200}$$

$$I_B = 25 \mu\text{A}$$


At input side

$$V_{BB} = I_B R_B + V_{BE}$$

$$= (25\text{mA}) (100\text{k}\Omega) + 1\text{V}$$


$$V_{BB} = 3.5 \text{ V}$$

8. Ans. (2)

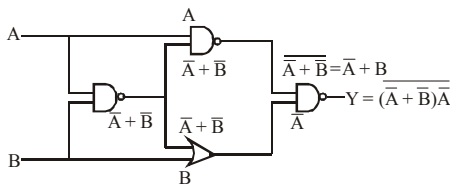

$$\begin{aligned}
 Y &= \overline{(\overline{A+B})\overline{A}} \\
 &= \overline{\overline{A+B}} \\
 &= A(\overline{A+B}) \\
 &= A(A+\overline{B}) \\
 &= A+A\overline{B} = A\overline{B}
 \end{aligned}$$

9. Ans. (3)

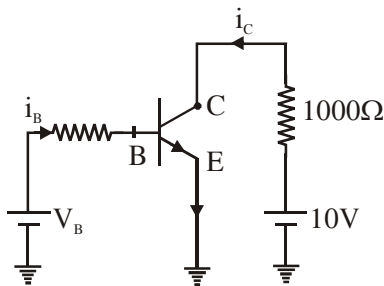

Sol.


At saturation state,  $V_{CE}$  becomes zero

$$\Rightarrow i_C = \frac{10V}{1000\Omega} = 10mA$$

now current gain factor  $\beta = \frac{i_C}{i_B}$

$$\Rightarrow i_B = \frac{10mA}{250} = 40\mu A$$

10. Ans. (3)

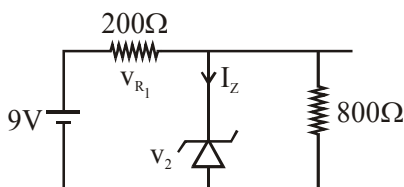


Sol.

$$\begin{aligned}
 9 &= V_Z + V_{R_1} \\
 V_Z &= 5.6 V \\
 V_{R_1} &= 9 - 5.6
 \end{aligned}$$

$$V_{R_1} = 3.4$$

$$I_{R_1} = \frac{V_{R_1}}{R} = \frac{3.4}{200}$$

$$I_{R_1} = 17 \text{ mA}$$

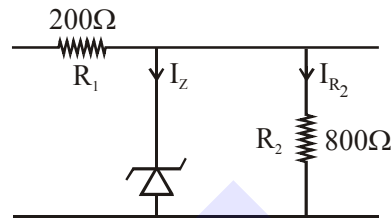

$$V_Z = V_{R_2} = I_{R_2}(R_2)$$

$$\frac{5.6}{800} = I_{R_2}$$

$$I_{R_2} = 7mA$$

$$\begin{aligned}
 I_Z &= (17 - 7) \text{ mA} \\
 &= 10 \text{ mA}
 \end{aligned}$$

11. Ans. (1)


Sol. Method 1

Truth table can be formed as

A	B	Equivalent
0	0	0
0	1	1
1	0	1
1	1	1

Hence the Equivalent is "OR" gate.

Method 2

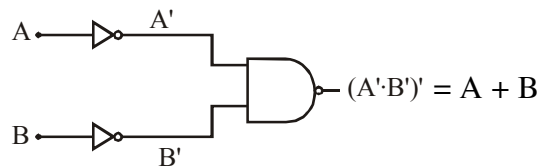

(OR GATE)

**12. Ans. (4)****Sol.** input current =  $15 \times 10^{-6}$ output current =  $3 \times 10^{-3}$ 

resistance output = 1000

$$V_{\text{input}} = 10 \times 10^{-3}$$

$$\text{Now } V_{\text{input}} = r_{\text{input}} \times i_{\text{input}}$$

$$10 \times 10^{-3} = r_{\text{input}} \times 15 \times 10^{-6}$$

$$r_{\text{input}} = \frac{2000}{3} = 0.67 \text{ K}\Omega.$$

$$\text{voltage gain} = \frac{V_{\text{output}}}{V_{\text{input}}} = \frac{1000 \times 3 \times 10^{-3}}{10 \times 10^{-3}} = 300$$

Option (4)

**13. Ans. (2)****Sol.** At  $V_B = 8\text{V}$ 

$$i_L = \frac{6 \times 10^{-3}}{4} = 1.5 \times 10^{-3} \text{ A}$$

$$i_R = \frac{8 - 6 \times 10^{-3}}{1} = 2 \times 10^{-3} \text{ A}$$

$$\therefore i_{\text{zener diode}} = i_R - i_{\text{load}} \\ = 0.5 \times 10^{-3} \text{ A}$$

At  $V_B = 16\text{V}$ 

$$i_L = 1.5 \times 10^{-3} \text{ A}$$

$$i_R = \frac{(16 - 6) \times 10^{-3}}{1} = 10 \times 10^{-3} \text{ A}$$

$$\therefore i_{\text{zener diode}} = i_R - i_L \\ = 8.5 \times 10^{-3} \text{ A}$$

**14. Ans. (4)****Sol.**  $A_v \times \beta = P_{\text{gain}}$ 


$$60 = 10 \log_{10} \left( \frac{P}{P_0} \right)$$

$$P = 10^6 = \beta^2 \times \frac{R_{\text{out}}}{R_{\text{in}}}$$

$$= \beta^2 \times \frac{10^4}{100}$$

$$\beta^2 = 10^4$$

$$\beta = 100$$

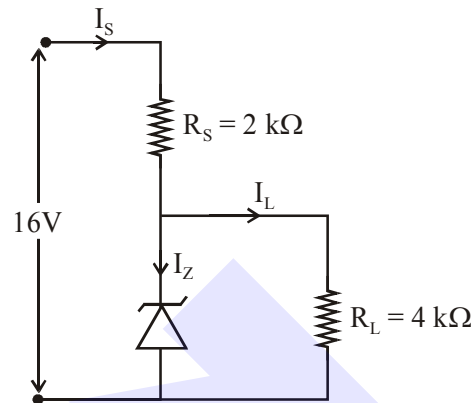**15. Ans. (2)****Sol.** Maximum current will flow from zener if input voltage is maximum.

When zener diode works in breakdown state, voltage across the zener will remain same.

$$\therefore V_{\text{across } 4\text{k}\Omega} = 6\text{V}$$

$$\therefore \text{Current through } 4\text{k}\Omega = \frac{6}{4000} \text{ A} = \frac{6}{4} \text{ mA}$$


Since input voltage = 16V

$$\therefore \text{Potential difference across } 2\text{k}\Omega = 10\text{V}$$

$$\therefore \text{Current through } 2\text{k}\Omega = \frac{10}{2000} = 5\text{mA}$$

$$\therefore \text{Current through zener diode} \\ = (I_S - I_L) = 3.5 \text{ mA}$$

16. Ans. (1)

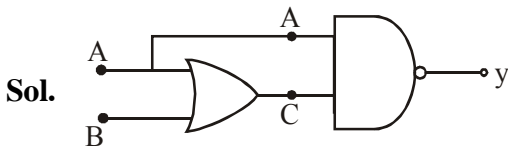

$$C = A + B$$

$$\text{and } y = \overline{A.C}$$

A	B	C = (A + B)	A.C.	y = $\overline{A.C}$
0	0	0	0	1
0	1	1	0	1
1	0	1	1	0
1	1	1	1	0

17. Ans. (3)

Sol.

$$V_{\text{gain}} = \left( \frac{\Delta I_C}{\Delta I_B} \right) \frac{R_{\text{out}}}{R_{\text{in}}}$$

$$= \left( \frac{5 \times 10^{-3}}{100 \times 10^{-6}} \right) \times 10^3$$

$$= \frac{1}{20} \times 10^6 = 5 \times 10^4$$

$$P_{\text{gain}} = \left( \frac{\Delta I_C}{\Delta I_b} \right) (V_{\text{gain}})$$

$$= \left( \frac{5 \times 10^{-3}}{100 \times 10^{-6}} \right) (5 \times 10^4)$$

$$= 2.5 \times 10^6$$