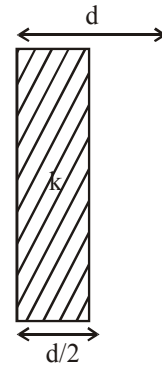



CAPACITOR

- Two equal capacitors are first connected in series and then in parallel. The ratio of the equivalent capacities in the two cases will be:
 - 4 : 1
 - 2 : 1
 - 1 : 4
 - 1 : 2
- An electron with kinetic energy K_1 enters between parallel plates of a capacitor at an angle ' α ' with the plates. It leaves the plates at angle ' β ' with kinetic energy K_2 . Then the ratio of kinetic energies $K_1 : K_2$ will be :
 - $\frac{\sin^2 \beta}{\cos^2 \alpha}$
 - $\frac{\cos^2 \beta}{\cos^2 \alpha}$
 - $\frac{\cos \beta}{\cos \alpha}$
 - $\frac{\cos \beta}{\sin \alpha}$
- Consider the combination of 2 capacitors C_1 and C_2 , with $C_2 > C_1$, when connected in parallel, the equivalent capacitance is $\frac{15}{4}$ time the equivalent capacitance of the same connected in series. Calculate the ratio of capacitors, $\frac{C_2}{C_1}$.
 - $\frac{15}{11}$
 - $\frac{111}{80}$
 - $\frac{29}{15}$
 - $\frac{15}{4}$
- For changing the capacitance of a given parallel plate capacitor, a dielectric material of dielectric constant K is used, which has the same area as the plates of the capacitor. The thickness of the dielectric slab is $\frac{3}{4}d$, where 'd' is the separation between the plates of parallel plate capacitor. The new capacitance (C') in terms of original capacitance (C_0) is given by the following relation :
 - $C' = \frac{3+K}{4K} C_0$
 - $C' = \frac{4+K}{3} C_0$
 - $C' = \frac{4K}{K+3} C_0$
 - $C' = \frac{4}{3+K} C_0$

- In a parallel plate capacitor set up, the plate area of capacitor is 2 m^2 and the plates are separated by 1 m . If the space between the plates are filled with a dielectric material of thickness 0.5 m and area 2 m^2 (see fig.) the capacitance of the set-up will be _____ ϵ_0 . (Dielectric constant of the material = 3.2) (Round off to the Nearest Integer)




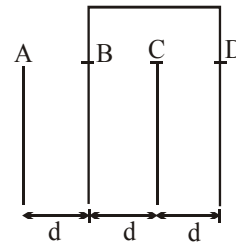- Four identical rectangular plates with length, $l = 2 \text{ cm}$ and breadth, $b = \frac{3}{2} \text{ cm}$ are arranged as shown in figure. The equivalent capacitance between A and C is $\frac{x\epsilon_0}{d}$. The value of x is _____. (Round off to the Nearest Integer)




- A parallel plate capacitor whose capacitance C is 14 pF is charged by a battery to a potential difference $V = 12 \text{ V}$ between its plates. The charging battery is now disconnected and a porcelain plate with $k = 7$ is inserted between the plates, then the plate would oscillate back and forth between the plates with a constant mechanical energy of _____ pJ . (Assume no friction)

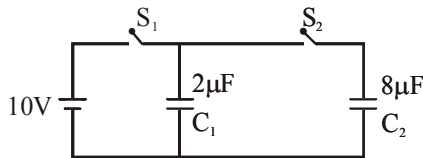8. A $2 \mu\text{F}$ capacitor C_1 is first charged to a potential difference of 10 V using a battery. Then the battery is removed and the capacitor is connected to an uncharged capacitor C_2 of $8 \mu\text{F}$. The charge in C_2 on equilibrium condition is _____ μC . (Round off to the Nearest Integer)



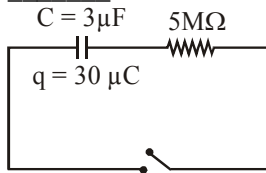9. The circuit shown in the figure consists of a charged capacitor of capacity $3 \mu\text{F}$ and a charge of $30 \mu\text{C}$. At time $t = 0$, when the key is closed, the value of current flowing through the $5 \text{ M}\Omega$ resistor is ' x ' μA . The value of ' x ' to the nearest integer is _____.



10. A parallel plate capacitor has plate area 100 m^2 and plate separation of 10 m . The space between the plates is filled up to a thickness 5 m with a material of dielectric constant of 10 . The resultant capacitance of the system is ' x ' pF . The value of $\epsilon_0 = 8.85 \times 10^{-12} \text{ F.m}^{-1}$. The value of ' x ' to the nearest integer is _____.
11. A parallel plate capacitor with plate area ' A ' and distance of separation ' d ' is filled with a dielectric. What is the capacity of the capacitor when permittivity of the dielectric varies as :

$$\epsilon(x) = \epsilon_0 + kx, \text{ for } \left(0 < x \leq \frac{d}{2}\right)$$

$$\epsilon(x) = \epsilon_0 + k(d - x), \text{ for } \left(\frac{d}{2} \leq x \leq d\right)$$

$$(1) \left(\epsilon_0 + \frac{kd}{2}\right)^{2/kA}$$

$$(2) \frac{kA}{2 \ln \left(\frac{2\epsilon_0 + kd}{2\epsilon_0}\right)}$$


$$(3) 0$$

$$(4) \frac{kA}{2} \ln \left(\frac{2\epsilon_0}{2\epsilon_0 - kd}\right)$$

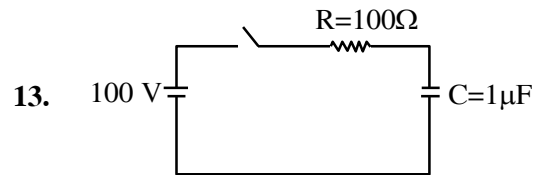12. If q_f is the free charge on the capacitor plates and q_b is the bound charge on the dielectric slab of dielectric constant k placed between the capacitor plates, then bound charge q_b can be expressed as :

$$(1) q_b = q_f \left(1 - \frac{1}{\sqrt{k}}\right) \quad (2) q_b = q_f \left(1 - \frac{1}{k}\right)$$

$$(3) q_b = q_f \left(1 + \frac{1}{\sqrt{k}}\right) \quad (4) q_b = q_f \left(1 + \frac{1}{k}\right)$$




13.

A capacitor of capacitance $C = 1 \mu\text{F}$ is suddenly connected to a battery of 100 volt through a resistance $R = 100 \Omega$. The time taken for the capacitor to be charged to get 50 V is :

[Take $\ln 2 = 0.69$]

- (1) $1.44 \times 10^{-4} \text{ s}$ (2) $3.33 \times 10^{-4} \text{ s}$
 (3) $0.69 \times 10^{-4} \text{ s}$ (4) $0.30 \times 10^{-4} \text{ s}$

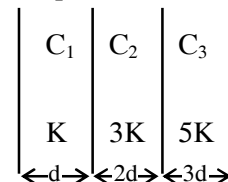14. In the reported figure, a capacitor is formed by placing a compound dielectric between the plates of parallel plate capacitor. The expression for the capacity of the said capacitor will be :
 (Given area of plate = A)



- (1) $\frac{15 K \epsilon_0 A}{34 d}$ (2) $\frac{15 K \epsilon_0 A}{6 d}$
 (3) $\frac{25 K \epsilon_0 A}{6 d}$ (4) $\frac{9 K \epsilon_0 A}{6 d}$

15. Two capacitors of capacities $2C$ and C are joined in parallel and charged up to potential V . The battery is removed and the capacitor of capacity C is filled completely with a medium of dielectric constant K . The potential difference across the capacitors will now be :


$$(1) \frac{V}{K+2}$$

$$(2) \frac{V}{K}$$

$$(3) \frac{3V}{K+2}$$


$$(4) \frac{3V}{K}$$

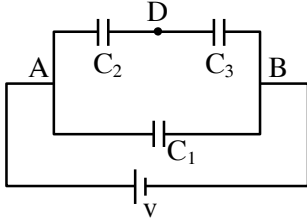20. Three capacitors $C_1 = 2\mu\text{F}$, $C_2 = 6\mu\text{F}$ and $C_3 = 12\mu\text{F}$ are connected as shown in figure. Find the ratio of the charges on capacitors C_1 , C_2 and C_3 respectively :



- (1) 2 : 1 : 1 (2) 2 : 3 : 3
 (3) 1 : 2 : 2 (4) 3 : 4 : 4

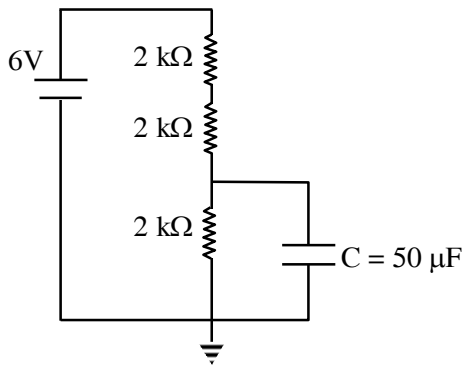21. A capacitor of $50\mu\text{F}$ is connected in a circuit as shown in figure. The charge on the upper plate of the capacitor is _____ μC .



22. A parallel plate capacitor of capacitance $200\mu\text{F}$ is connected to a battery of 200V . A dielectric slab of dielectric constant 2 is now inserted into the space between plates of capacitor while the battery remain connected. The change in the electrostatic energy in the capacitor will be _____ J.

23. A capacitor is connected to a 20V battery through a resistance of 10Ω . It is found that the potential difference across the capacitor rises to 2V in $1\mu\text{s}$. The capacitance of the capacitor is


..... μF . Given : $\ln\left(\frac{10}{9}\right) = 0.105$

- (1) 9.52 (2) 0.95
 (3) 0.105 (4) 1.85

SOLUTION


1. Official Ans. by NTA (3)

Sol. For series combination

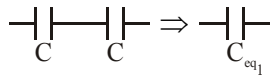

$$\frac{1}{C_{eq1}} = \frac{1}{C} + \frac{1}{C} \Rightarrow C_{eq1} = \frac{C}{2}$$

For parallel combination

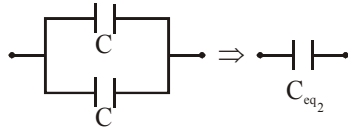


$$C_{eq2} = C + C \Rightarrow C_{eq2} = 2C$$

$$\Rightarrow \frac{C_{eq1}}{C_{eq2}} = \frac{(C/2)}{2C} = \frac{1}{4} = 1 : 4$$

2. Official Ans. by NTA (2)

Sol.

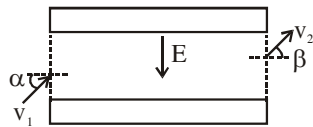

velocity along the plate will not change.

$$\therefore v_1 \cos \alpha = v_2 \cos \beta$$

$$\frac{K_1}{K_2} \Rightarrow \frac{v_1^2}{v_2^2} = \frac{\cos^2 \beta}{\cos^2 \alpha}$$

3. Official Ans. by NTA (BONUS)

Sol. When connected in parallel

$$C_{eq} = C_1 + C_2$$

When in series

$$C'_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_1 + C_2 = \frac{15}{4} \left(\frac{C_1 C_2}{C_1 + C_2} \right)$$

$$4(C_1 + C_2)^2 = 15 C_1 C_2$$

$$4 C_1^2 + 4 C_2^2 - 7 C_1 C_2 = 0$$

dividing by C_1^2

$$4 \left(\frac{C_2}{C_1} \right)^2 - \frac{7 C_2}{C_1} + 4 = 0$$

Let $\frac{C_2}{C_1} = x$


$$4x^2 - 7x + 4 = 0$$

$$b^2 - 4ac = 49 - 64 < 0$$

No solution exists

4. Official Ans. by NTA (3)

Sol.

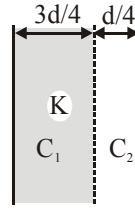

$$C_0 = \frac{\epsilon_0 A}{d}$$

$C' = C_1$ and C_2 in series.

$$\text{i.e. } \frac{1}{C'} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{1}{C'} = \frac{(3d/4)}{\epsilon_0 K A} + \frac{d/4}{\epsilon_0 A}$$

$$\frac{1}{C'} = \frac{d}{4 \epsilon_0 A} \left(\frac{3+K}{K} \right)$$

$$C' = \frac{4KC_0}{(3+K)}$$

5. Official Ans. by NTA (3)


Sol. Ans. (3)

$$C = \frac{\epsilon_0 A}{\frac{d}{2K} + \frac{d}{2}} = \frac{2\epsilon_0 A}{\frac{d}{K} + d}$$

$$= \frac{2 \times 2\epsilon_0}{\frac{1}{3.2} + 1} = \frac{4 \times 3.2}{4.2} \epsilon_0 = 3.04 \epsilon_0$$

6. Official Ans. by NTA (2)

Sol.

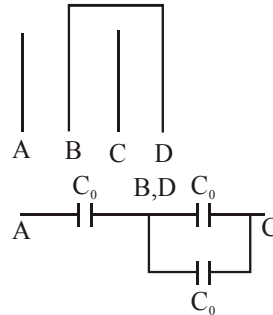

$$C_{eq} = \frac{2C_0}{3} = \frac{2 \epsilon_0 A}{3 d}$$

$$C_{eq} = \frac{2 \epsilon_0}{3d} \times \left(2 \times \frac{3}{2} \right) = 2 \quad (\because A = lb = 2 \times \frac{3}{2})$$

7. Official Ans. by NTA (864)

Sol. $U_i = \frac{1}{2} \times 14 \times 12 \times 12 \text{ pJ} \quad (\because U = \frac{1}{2} CV^2)$

$$= 1008 \text{ pJ}$$

$$U_f = \frac{1008}{7} \text{ pJ} = 144 \text{ pJ} \quad (\because C_m = kC_0)$$

Mechanical energy = ΔU

$$= 1008 - 144 = 864 \text{ pJ}$$

8. Official Ans. by NTA (16)

Sol. $20 = (C_1 + C_2) V \Rightarrow V = 2$ volt.


$$Q_2 = C_2 V = 16 \mu\text{C} = 16$$

9. Official Ans. by NTA (2)

Sol. $i_0 = \frac{V}{R} = \frac{30/3}{5 \times 10^6} = 2 \times 10^{-6}$

$$\therefore \text{Ans.} = 2.00$$

10. Official Ans. by NTA (161)

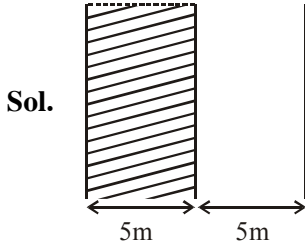

$$A = 100 \text{ m}^2$$

Using $C = \frac{k \epsilon_0 A}{d}$


$$C_1 = \frac{10 \epsilon_0 (100)}{5} = 200 \epsilon_0$$

$$C_2 = \frac{\epsilon_0 (100)}{5} = 20 \epsilon_0$$

$$C_1 \text{ \& } C_2 \text{ are in series so } C_{\text{eqv.}} = \frac{C_1 C_2}{C_1 + C_2}$$

$$= \frac{4000 \epsilon_0}{220} = 160.9 \times 10^{-12} \approx 161 \text{ pF}$$

11. Official Ans. by NTA (2)

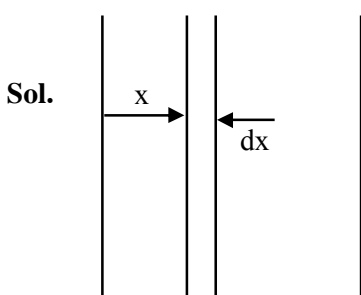

Taking an element of width dx at a distance x ($x < d/2$) from left plate

$$dc = \frac{(\epsilon_0 + kx)A}{dx}$$

Capacitance of half of the capacitor


$$\frac{1}{C} = \int_0^{d/2} \frac{1}{dc} = \frac{1}{A} \int_0^{d/2} \frac{dx}{\epsilon_0 + kx}$$

$$\frac{1}{C} = \frac{1}{kA} \ln \left(\frac{\epsilon_0 + kd/2}{\epsilon_0} \right)$$

Capacitance of second half will be same

$$C_{\text{eq}} = \frac{C}{2} = \frac{kA}{2 \ln \left(\frac{2\epsilon_0 + kd}{2\epsilon_0} \right)}$$

12. Official Ans. by NTA (2)

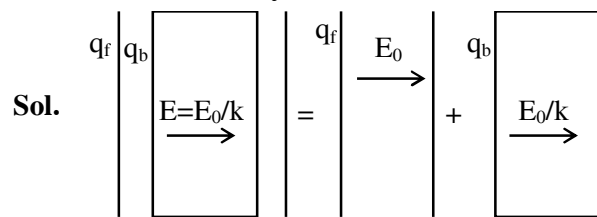

When a dielectric is inserted in a capacitor

Due to free charge $\vec{E} = \vec{E}_0$ only

After dielectric $E' = \frac{E_0}{k}$

$$q_B = q_f \left(1 - \frac{1}{k} \right)$$

13. Official Ans. by NTA (3)

Sol. $V = V_0 \left(1 - e^{-\frac{t}{RC}} \right)$

$$50 = 100 \left(1 - e^{-\frac{t}{RC}} \right)$$


$$t = 0.69 \times 10^{-4} \text{ sec.}$$

14. Official Ans. by NTA (1)


Sol. $\frac{1}{C_{\text{eff}}} = \frac{d}{K \epsilon_0 A} + \frac{2d}{3K \epsilon_0 A} + \frac{3d}{5K \epsilon_0 A}$

$$C_{\text{eff}} = \frac{15K \epsilon_0 A}{34d}$$

15. Official Ans. by NTA (3)

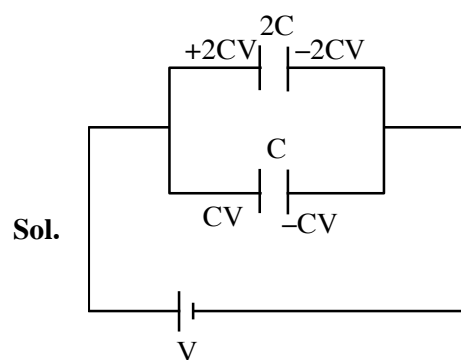


Now,

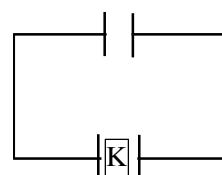

$$V_c = \frac{2CV + CV}{KC + 2C} = \frac{3V}{K + 2}$$

16. Official Ans. by NTA (3)

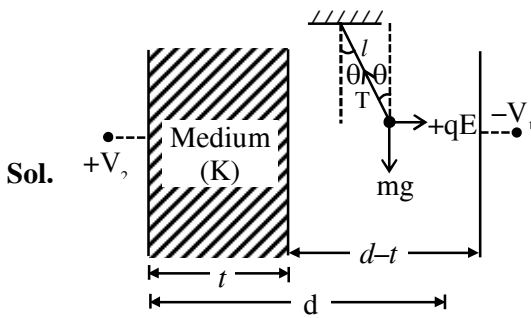


Let E be electric field in air

$$T \sin\theta = qE$$

$$T \cos\theta = mg$$

$$\tan\theta = \frac{qE}{mg}$$

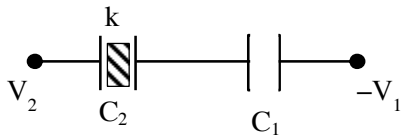

$$Q = \left[\frac{C_1 C_2}{C_1 + C_2} \right] [V_1 + V_2]$$

$$E = \frac{Q}{A\epsilon_0} = \left[\frac{C_1 C_2}{C_1 + C_2} \right] \frac{[V_1 + V_2]}{A\epsilon_0}$$

$$C_1 = \frac{\epsilon_0 A}{d-t} \Rightarrow E = \frac{C_2 [V_1 + V_2]}{(C_1 + C_2)(d-t)}$$

$$\text{Now } \theta = \tan^{-1} \left[\frac{q.E}{mg} \right]$$

$$\theta = \tan^{-1} \left[\frac{q}{mg} \times \frac{C_2 (V_1 + V_2)}{(C_1 + C_2)(d-t)} \right]$$

17. Official Ans. by NTA (3)

Sol. $\rho = 200 \Omega\text{m}$

$$C = 2 \times 10^{-12} \text{ F}$$

$$V = 40 \text{ V}$$

$$K = 56$$

$$i = \frac{q}{\rho k \epsilon_0} = \frac{q_0}{\rho k \epsilon_0} e^{-\frac{t}{\rho k \epsilon_0}}$$

$$i_{\text{max}} = \frac{2 \times 10^{-12} \times 40}{200 \times 50 \times 8.85 \times 10^{-12}}$$


$$= \frac{80}{10^4 \times 8.85} = 903 \mu\text{A} = 0.9 \text{ mA}$$

Option (3)

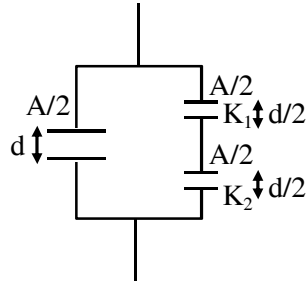18. Official Ans. by NTA (1)


$$\text{Sol. } C_{\text{eq}} = \frac{\frac{A}{2} \epsilon_0}{d} + \frac{A \epsilon_0}{d} \frac{K_1 K_2}{K_1 + K_2}$$

$$= \frac{A \epsilon_0}{d} \left(\frac{1}{2} + \frac{K_1 K_2}{K_1 + K_2} \right)$$



19. Official Ans. by NTA (1)

Sol. On simplifying circuit we get

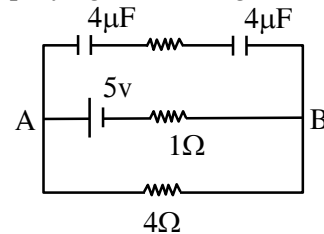

No current in upper wire.


$$\therefore V_{AB} = \frac{5}{4+1} \times 4 = 4 \text{ v.}$$

$$\therefore \theta = (C_{\text{eq}})V$$

$$\Rightarrow 2 \times 4 = 8 \mu\text{C}$$

20. Official Ans. by NTA (3)

Sol.

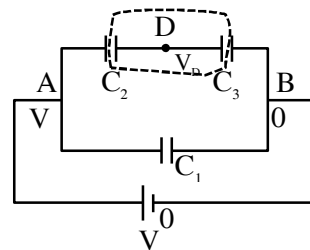

$$(V_D - V) C_2 + (V_D - 0) C_3 = 0$$

$$(V_D - V) 6 + (V_D - 0) 12 = 0$$

$$V_D - V + 2V_D = 0$$

$$V_D = \frac{V}{3}$$

$$q_2 = (V - V_D) C_2 = \left(V - \frac{V}{3} \right) (6 \mu\text{F})$$

$$q_2 = (4V) \mu\text{F}$$


$$q_3 = (V_D - 0) C_3 = \frac{V}{3} \times 12 \mu\text{F} = 4V \mu\text{F}$$

$$q_1 = (V - 0) C_1 = V(2 \mu\text{F})$$

$$q_1 : q_2 : q_3 = 2 : 4 : 4$$

$$q_1 : q_2 : q_3 = 1 : 2 : 2$$

21. Official Ans. by NTA (100)

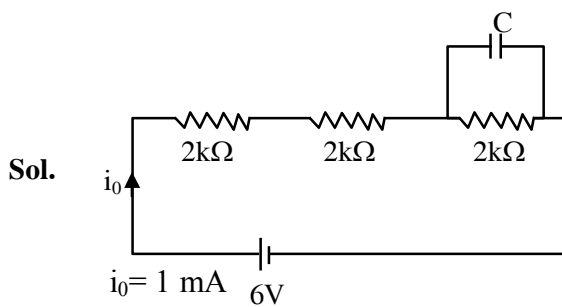

Pot. Diff. across each resistor = 2V

$$q = CV$$

$$= 50 \times 10^{-6} \times 2 = 100 \times 10^{-6} = 100 \mu\text{C}$$

22. Official Ans. by NTA (4)

Sol. $\Delta U = \frac{1}{2}(\Delta C)V^2$

$$\Delta U = \frac{1}{2}(KC - C)V^2$$

$$\Delta U = \frac{1}{2}(2 - 1)CV^2$$

$$\Delta U = \frac{1}{2} \times 200 \times 10^{-6} \times 200 \times 200$$

$$\Delta U = 4 \text{ J}$$

23. Official Ans. by NTA (2)

Sol. $V = V_0(1 - e^{-t/RC})$

$$2 = 20(1 - e^{-t/RC})$$

$$\frac{1}{10} = 1 - e^{-t/RC}$$

$$e^{-t/RC} = \frac{9}{10}$$

$$e^{t/RC} = \frac{10}{9}$$

$$\frac{t}{RC} = \ln\left(\frac{10}{9}\right) \Rightarrow C = \frac{t}{R \ln\left(\frac{10}{9}\right)}$$

$$C = \frac{10^{-6}}{10 \times 105} = .95 \mu\text{F}$$

Option (2)